

B-005-001-006 (C)

A kilohm is:

- A 0.001 ohm
- B 10 ohms
- C 1000 ohms
- D 0.1 ohm

B-005-001-007 (B)

6.6 kilovolts is equal to:

- A 66 000 volts
- B 6600 volts
- C 660 volts
- D 66 volts

B-005-001-008 (C)

A current of one quarter ampere may be written as:

- A 0.25 milliampere
- B 250 microamperes
- C 250 milliamperes
- D 0.5 amperes

B-005-001-009 (D)

How many millivolts are equivalent to two volts?

- A 0.000002
- B 2 000 000
- C 0.002
- D 2 000

B-005-001-010 (A)

One megahertz is equal to:

- A 1 000 kHz
- B 100 kHz
- C 0.001 Hz
- D 10 Hz

B-005-001-011 (C)

An inductance of 10 000 microhenrys may be stated correctly as:

- A 10 henrys
- B 1 000 henrys
- C 10 millihenrys
- D 100 millihenrys

B-005-002-001 (A)

Name three good electrical conductors.

- A Gold, silver, aluminum
- B Gold, silver, wood
- C Copper, aluminum, paper
- D Copper, gold, mica

B-005-002-002 (B)

Name four good electrical insulators.

- A Glass, wood, copper, porcelain
- B Glass, air, plastic, porcelain
- C Plastic, rubber, wood, carbon
- D Paper, glass, air, aluminum

B-005-002-003 (B)

Why do resistors sometimes get hot when in use?

- A They absorb magnetic energy which makes them hot
- B Some electrical energy passing through them is lost as heat
- C Their reactance makes them heat up
- D Hotter circuit components nearby heat them up

B-005-002-004 (A)

What is the best conductor among the following materials?

- A copper
- B carbon
- C silicon
- D aluminium

B-005-002-005 (B)

Which type of material listed will most readily allow an electric current to flow?

- A a dielectric
- B a conductor
- C an insulator
- D a semiconductor

B-005-002-006 (D)

A length of metal is connected in a circuit and is found to conduct electricity very well. It would be best described as having a:

- A high resistance
- B high wattage
- C low wattage
- D low resistance

B-005-002-007 (C)

The letter "R" is the symbol for:

- A reluctance
- B reactance
- C resistance
- D impedance

B-005-002-008 (B)

The reciprocal of resistance is:

- A permeability
- B conductance
- C reactance
- D reluctance

B-005-002-009 (A)

Voltage drop means:

- A the voltage developed across the terminals of a component
- B any point in a radio circuit which has zero voltage
- C the difference in voltage at output terminals of a transformer
- D the voltage which is dissipated before useful work is accomplished

B-005-002-010 (C)

The resistance of a conductor changes with:

- A current
- B humidity
- C temperature
- D voltage

B-005-002-011 (A)

The most common material used to make a resistor is:

- A carbon
- B gold
- C mica
- D lead

B-005-003-001 (A)

What is the word used to describe the rate at which electrical energy is used?

- A Power
- B Current
- C Voltage
- D Resistance

B-005-003-002 (C)

If you have light bulbs marked 40 watts, 60 watts and 100 watts, which one will use electrical energy the fastest?

- A The 40 watt bulb
- B The 60 watt bulb
- C The 100 watt bulb
- D They will all be the same

B-005-003-003 (B)

What is the basic unit of electrical power?

- A The ohm
- B The watt
- C The ampere
- D The volt

B-005-003-004 (C)

Which electrical circuit will have no current?

- A A complete circuit
- B A closed circuit
- C An open circuit
- D A short circuit

B-005-003-005 (B)

Which electrical circuit draws too much current?

- A An open circuit
- B A short circuit
- C A dead circuit
- D A closed circuit

B-005-003-006 (B)

Power is expressed in:

- A ohms
- B watts
- C volts
- D amperes

B-005-003-007 (C)

Which of the following two quantities should be multiplied together to find power?

- A Voltage and inductance
- B Resistance and capacitance
- C Voltage and current
- D Inductance and capacitance

B-005-003-008 (C)

Which two electrical units multiplied together give the unit "watts"?

- A Farads and henrys
- B Amperes and henrys
- C Volts and amperes
- D Volts and farads

B-005-003-009 (B)

A resistor in a circuit becomes very hot and starts to burn. This is because the resistor is dissipating too much:

- A current
- B power
- C voltage
- D resistance

B-005-003-010 (A)

High power resistors are usually large with heavy leads. The size aids the operation of the resistor by:

- A allowing heat to dissipate more readily
- B allowing higher voltage to be handled
- C increasing the effective resistance of the resistor
- D making it shock proof

B-005-003-011 (A)

The resistor that could dissipate the most heat would be marked:

- A 20 watts
- B 100 ohms
- C 2 ohms
- D 0.5 watt

B-005-004-001 (B)

If a current of 2 amperes flows through a 50-ohm resistor, what is the voltage across the resistor?

- A 25 volts
- B 100 volts
- C 48 volts
- D 52 volts

B-005-004-002 (C)

How is the current in a DC circuit calculated when the voltage and resistance are known?

- A Current equals resistance divided by voltage
- B Current equals power divided by voltage
- C Current equals voltage divided by resistance
- D Current equals resistance multiplied by voltage

B-005-004-003 (C)

How is the resistance in a DC circuit calculated when the voltage and current are known?

- A Resistance equals power divided by voltage
- B Resistance equals current divided by voltage
- C Resistance equals voltage divided by current
- D Resistance equals current multiplied by voltage

B-005-004-004 (A)

How is the voltage in a DC circuit calculated when the current and resistance are known?

- A Voltage equals current multiplied by resistance
- B Voltage equals current divided by resistance
- C Voltage equals resistance divided by current
- D Voltage equals power divided by current

B-005-004-005 (C)

If a 12-volt battery supplies 0.25 ampere to a circuit, what is the circuit's resistance?

- A 12 ohms
- B 0.25 ohm
- C 48 ohms
- D 3 ohms

B-005-004-006 (C)

Calculate the value of resistance necessary to drop 100 volts with current flow of 0.8 milliamperes:

- A 1250 ohms
- B 1.25 kilohms
- C 125 kilohms
- D 125 ohms

B-005-004-007 (C)

The voltage required to force a current of 4.4 amperes through a resistance of 50 ohms is:

- A 22.0 volts
- B 0.220 volt
- C 220 volts
- D 2220 volts

B-005-004-008 (C)

A lamp has a resistance of 30 ohms and a 6 volt battery is connected. The current flow will be:

- A 0.5 ampere
- B 0.005 ampere
- C 0.2 ampere
- D 2 amperes

B-005-004-009 (C)

What voltage would be needed to supply a current of 200 milliamperes, to operate an electric lamp which has a resistance of 25 ohms?

- A 175 volts
- B 225 volts
- C 5 volts
- D 8 volts

B-005-004-010 (C)

The resistance of a circuit can be found by using one of the following:

- A $R = E/R$
- B $R = E \times I$
- C $R = E/I$
- D $R = I/E$

B-005-004-011 (C)

If a 3 volt battery supplies 300 milliamperes to a circuit, the circuit resistance is:

- A 5 ohms
- B 3 ohms
- C 10 ohms
- D 9 ohms

B-005-005-001 (D)

In a parallel circuit with a voltage source and several branch resistors, how is the total current related to the current in the branch resistors?

- A It equals the average of the branch current through each resistor
- B It decreases as more parallel resistors are added to the circuit
- C It is the sum of each resistor's voltage drop multiplied by the total number of resistors
- D It equals the sum of the branch current through each resistor

B-005-005-002 (B)

Three resistors, respectively rated at 10, 15 and 20 ohms are connected in parallel across a 6-volt battery. Which statement is true?

- A The voltage drop across the 20 ohm resistance is greater than the voltage across the 10 ohm resistance
- B The current through the 10 ohms, 15 ohms and 20 ohms separate resistances, when added together, equals the total current drawn from the battery
- C The current flowing through the 10 ohm resistance is less than that flowing through the 20 ohm resistance
- D The voltage drop across each resistance added together equals 6 volts

B-005-005-003 (B)

Total resistance in a parallel circuit:

- A depends upon the applied voltage
- B is always less than the smallest resistance
- C depends upon the voltage drop across each branch
- D could be equal to the resistance of one branch

B-005-005-004 (A)

Two resistors are connected in parallel and are connected across a 40 volt battery. If each resistor is 1000 ohms, the total current is:

- A 80 milliamperes
- B 40 milliamperes
- C 80 amperes
- D 40 amperes

B-005-005-005 (B)

The total resistance of resistors connected in series is:

- A equal to the lowest resistance present
- B greater than the resistance of any one resistor
- C less than the resistance of any one resistor
- D equal to the highest resistance present

B-005-005-006 (B)

Five 10 ohm resistors connected in series equals:

- A 1 ohm
- B 50 ohms
- C 5 ohms
- D 10 ohms

B-005-005-007 (A)

Which series combination of resistors would replace a single 120 ohm resistor?

- A Five 24 ohm
- B Six 22 ohm
- C Two 62 ohm
- D Five 100 ohm

B-005-005-008 (D)

If ten resistors of equal value were wired in parallel, the total resistance would be:

- A $10 / R$
- B $10 \times R$
- C $10 + R$
- D $R / 10$

B-005-005-009 (D)

The total resistance of four 68 ohm resistors wired in parallel is:

- A 12 ohms
- B 34 ohms
- C 272 ohms
- D 17 ohms

B-005-005-010 (B)

Two resistors are in parallel. Resistor A carries twice the current of resistor B, which means that:

- A B has half the resistance of A
- B A has half the resistance of B
- C the voltage across B is twice that across A
- D the voltage across A is twice that across B

B-005-005-011 (C)

The total current in a parallel circuit is equal to the:

- A source voltage divided by the sum of the resistive elements
- B current in any one of the parallel branches
- C sum of the currents through all the parallel branches
- D source voltage divided by the value of one of the resistive elements

B-005-006-001 (C)

Why would a large size resistor be used instead of a smaller one of the same resistance?

- A For a higher current gain
- B For less impedance in the circuit
- C For greater power dissipation
- D For better response time

B-005-006-002 (C)

How many watts of electrical power are used by a 12 volt DC light bulb that draws 0.2 ampere?

- A 24 watts
- B 6 watts
- C 2.4 watts
- D 60 watts

B-005-006-003 (C)

The DC input power of a transmitter operating at 12 volts and drawing 500 milliamperes would be:

- A 500 watts
- B 12 watts
- C 6 watts
- D 20 watts

B-005-006-004 (A)

When two 500 ohm 1 watt resistors are connected in series, the maximum total power that can be dissipated by the resistors is:

- A 2 watts
- B 1 watt
- C 1/2 watt
- D 4 watts

B-005-006-005 (C)

When two 500 ohm 1 watt resistors are connected in parallel, they can dissipate a maximum total power of:

- A 1 watt
- B 4 watts
- C 2 watts
- D 1/2 watt

B-005-006-006 (C)

If the voltage applied to two resistors in series is doubled, how much will the total power change?

- A Double
- B No change
- C Increase four times
- D Decrease to half

B-005-006-007 (D)

Which combination of resistors could make up a 50 ohms dummy load capable of safely dissipating 5 watts?

- A Two 5-watt 100 ohms resistors in series
- B Two 2-watt 25 ohms resistors in series
- C Ten quarter-watt 500 ohms resistors in parallel
- D Four 2-watt 200 ohms resistors in parallel

B-005-006-008 (A)

A 12 volt light bulb is rated at a power of 30 watts. The current drawn would be:

- A 30/12 amperes
- B 18 amperes
- C 360 amperes
- D 12/30 amperes

B-005-006-009 (B)

If two 10 ohm resistors are connected in series with a 10 volt battery, the power consumption would be:

- A 100 watts
- B 5 watts
- C 10 watts
- D 20 watts

B-005-006-010 (B)

One advantage of replacing a 50 ohm resistor with a parallel combination of two similarly rated 100 ohm resistors is that the parallel combination will have:

- A lesser resistance and similar power rating
- B the same resistance but greater power rating
- C the same resistance but lesser power rating
- D greater resistance and similar power rating

B-005-006-011 (D)

Resistor wattage ratings are:

- A calculated according to physical size and tolerance rating
- B expressed in joules
- C variable in steps of one hundred
- D determined by heat dissipation qualities