

B-005-010-009 (A)

What property allows an RF bypass capacitor to have little effect on an audio circuit?

- A High reactance at low frequencies
- B Low reactance at high frequencies
- C High reactance at high frequencies
- D Low reactance at low frequencies

B-005-010-010 (D)

What property allows an RF choke coil to have little effect on signals meant to flow through the coil?

- A High reactance at low frequencies
- B Low reactance at high frequencies
- C High reactance at high frequencies
- D Low reactance at low frequencies

B-005-010-011 (D)

In general, the reactance of inductors increases with:

- A decreasing AC frequency
- B decreasing applied voltage
- C increasing applied voltage
- D increasing AC frequency

B-005-011-001 (D)

If no load is attached to the secondary winding of a transformer, what is current in the primary winding called?

- A Direct current
- B Latent current
- C Stabilizing current
- D Magnetizing current

B-005-011-002 (B)

A transformer operates a 6.3 volt 2 ampere light bulb from its secondary winding. The input power to the primary winding is approximately:

- A 3 watts
- B 13 watts
- C 6 watts
- D 8 watts

B-005-011-003 (B)

A transformer has a 240 volt primary that draws a current of 250 milliamperes from the mains supply. Assuming no losses and only one secondary, what current would be available from the 12 volt secondary?

- A 50 amperes
- B 5 amperes
- C 215 amperes
- D 25 amperes

B-005-011-004 (C)

In a mains power transformer, the primary winding has 250 turns, and the secondary has 500. If the input voltage is 120 volts, the likely secondary voltage is:

- A 610 V
- B 26 V
- C 240 V
- D 480 V

B-005-011-005 (B)

The strength of the magnetic field around a conductor in air is:

- A inversely proportional to the voltage on the conductor
- B directly proportional to the current in the conductor
- C inversely proportional to the diameter of the conductor
- D directly proportional to the diameter of the conductor

B-005-011-006 (A)

Maximum induced voltage in a coil occurs when:

- A current is going through its greatest rate of change
- B the current through the coil is of a DC nature
- C current is going through its least rate of change
- D the magnetic field around the coil is not changing

B-005-011-007 (C)

The voltage induced in a conductor moving in a magnetic field is at a maximum when the movement is:

- A parallel to the lines of force
- B made in a clockwise direction
- C perpendicular to the lines of force
- D made in a counter clockwise direction

B-005-011-008 (A)

A 100% efficient transformer has a turns ratio of 1/5. If the secondary current is 50 milliamperes, the primary current is:

- A 0.25 A
- B 2 500 mA
- C 0.01 A
- D 0.25 mA

B-005-011-009 (B)

A force of repulsion exists between two _____ magnetic poles.

- A negative
- B like
- C unlike
- D positive

B-005-011-010 (A)

A permanent magnet would most likely be made from:

- A steel
- B copper
- C aluminum
- D brass

B-005-011-011 (B)

The fact that energy transfer from primary to secondary windings in a power transformer is not perfect is indicated by:

- A high primary voltages
- B warm iron laminations
- C electrostatic shielding
- D large secondary currents

B-005-012-001 (B)

Resonance is the condition that exists when:

- A resistance is equal to the reactance
- B inductive reactance and capacitive reactance are equal
- C inductive reactance is the only opposition in the circuit
- D the circuit contains no resistance

B-005-012-002 (C)

Parallel tuned circuits offer:

- A zero impedance at resonance
- B an impedance equal to resistance of the circuit
- C high impedance at resonance
- D low impedance at resonance

B-005-012-003 (D)

Resonance is an electrical property used to describe:

- A an inductor
- B a set of parallel inductors
- C the results of tuning a varicap (varactor)
- D the frequency characteristic of a coil and capacitor circuit

B-005-012-004 (D)

A tuned circuit is formed from two basic components. These are:

- A resistors and transistors
- B directors and reflectors
- C diodes and transistors
- D inductors and capacitors

B-005-012-005 (B)

When a parallel coil-capacitor combination is supplied with AC of different frequencies, there will be one frequency where the impedance will be highest. This is the:

- A reactive frequency
- B resonant frequency
- C impedance frequency
- D inductive frequency

B-005-012-006 (B)

In a parallel-resonant circuit at resonance, the circuit has a:

- A high mutual inductance
- B high impedance
- C low impedance
- D low mutual inductance

B-005-012-007 (B)

In a series resonant circuit at resonance, the circuit has:

- A high mutual inductance
- B low impedance
- C high impedance
- D low mutual inductance

B-005-012-008 (D)

A coil and an air-spaced capacitor are arranged to form a resonant circuit. The resonant frequency will remain the same if we:

- A increase the area of plates in the capacitor
- B insert Mylar sheets between the plates of the capacitor
- C wind more turns on the coil
- D add a resistor to the circuit

B-005-012-009 (B)

Resonant circuits in a receiver are used to:

- A adjust voltage levels
- B select signal frequencies
- C filter direct current
- D increase power

B-005-012-010 (D)

Resonance is the condition that exists when:

- A inductive reactance is the only opposition in the circuit
- B the circuit contains no resistance
- C resistance is equal to the reactance
- D inductive reactance and capacitive reactance are equal and opposite in sign

B-005-012-011 (A)

When a series LCR circuit is tuned to the frequency of the source, the:

- A line current reaches maximum
- B line current lags the applied voltage
- C line current leads the applied voltage
- D impedance is maximum

B-005-013-001 (A)

How is a voltmeter usually connected to a circuit under test?

- A In parallel with the circuit
- B In series with the circuit
- C In quadrature with the circuit
- D In phase with the circuit

B-005-013-002 (A)

How is an ammeter usually connected to a circuit under test?

- A In series with the circuit
- B In quadrature with the circuit
- C In phase with the circuit
- D In parallel with the circuit

B-005-013-003 (A)

What does a multimeter measure?

- A Voltage, current and resistance
- B Resistance, capacitance and inductance
- C Resistance and reactance
- D SWR and power

B-005-013-004 (B)

The correct instrument to measure plate current or collector current of a transmitter is:

- A a voltmeter
- B an ammeter
- C an ohmmeter
- D a wattmeter

B-005-013-005 (D)

Which of the following meters would you use to measure the power supply current drawn by a small hand-held transistorized receiver?

- A An RF ammeter
- B An RF power meter
- C An electrostatic voltmeter
- D A DC ammeter

B-005-013-006 (D)

When measuring current drawn from a DC power supply, it is true to say that the meter will act in circuit as:

- A a perfect conductor
- B an extra current drain
- C an insulator
- D a low value resistance

B-005-013-007 (D)

When measuring the current drawn by a receiver from a power supply, the current meter should be placed:

- A in series with both receiver power leads
- B in parallel with both receiver power supply leads
- C in parallel with one of the receiver power leads
- D in series with one of the receiver power leads

B-005-013-008 (B)

Potential difference is measured by means of:

- A an ammeter
- B a voltmeter
- C a wattmeter
- D an ohmmeter

B-005-013-009 (A)

The instrument used for measuring the flow of electrical current is the:

- A ammeter
- B faradmeter
- C wattmeter
- D voltmeter

B-005-013-010 (D)

In measuring volts and amperes, the connections should be made with:

- A the voltmeter in series and ammeter in parallel
- B both voltmeter and ammeter in series
- C both voltmeter and ammeter in parallel
- D the voltmeter in parallel and ammeter in series

B-006-001-001 (A)

What connects your transceiver to your antenna?

- A A transmission line
- B The power cord
- C A ground wire
- D A dummy load

B-006-001-002 (D)

The characteristic impedance of a transmission line is determined by the:

- A length of the line
- B frequency at which the line is operated
- C load placed on the line
- D physical dimensions and relative positions of the conductors

B-006-001-003 (A)

The characteristic impedance of a 20 metre piece of transmission line is 52 ohms. If 10 metres were cut off, the impedance would be:

- A 52 ohms
- B 26 ohms
- C 39 ohms
- D 13 ohms

B-006-001-004 (C)

The characteristic impedance of a coaxial line:

- A is correct for only one size of line
- B is greater for larger diameter line
- C can be the same for different diameter line
- D changes significantly with the frequency of the energy it carries

B-006-001-005 (A)

What commonly available antenna transmission line can be buried directly in the ground for some distance without adverse effects?

- A Coaxial cable
- B 300 ohm twin-lead
- C 600 ohm open-wire line
- D 75 ohm twin-lead

B-006-001-006 (A)

The characteristic impedance of a transmission line is:

- A equal to the pure resistance which, if connected to the end of the line, will absorb all the power arriving along it
- B the impedance of a section of the line one wavelength long
- C the dynamic impedance of the line at the operating frequency
- D the ratio of the power supplied to the line to the power delivered to the load

B-006-001-007 (D)

A transmission line differs from an ordinary circuit or network in communications or signalling devices in one very important way. That important aspect is:

- A capacitive reactance
- B inductive reactance
- C resistance
- D propagation delay

B-006-001-008 (D)

The characteristic impedance of a parallel wire transmission line does not depend on the:

- A radius of the conductors
- B centre to centre distance between conductors
- C dielectric
- D velocity of energy on the line

B-006-001-009 (D)

If the impedance terminating a transmission line differs significantly from the characteristic impedance of the line, what will be observed at the input of the line?

- A An infinite impedance
- B A negative impedance
- C An impedance nearly equal to the characteristic impedance
- D Some value of impedance influenced by line length

B-006-001-010 (A)

What factors determine the characteristic impedance of a parallel-conductor antenna transmission line?

- A The distance between the centres of the conductors and the radius of the conductors
- B The distance between the centres of the conductors and the length of the line
- C The radius of the conductors and the frequency of the signal
- D The frequency of the signal and the length of the line

B-006-001-011 (A)

What factors determine the characteristic impedance of a coaxial antenna transmission line?

- A The ratio of the diameter of the inner conductor to the diameter of the outer shield
- B The diameter of the shield and the length of the line
- C The diameter of the shield and the frequency of the signal
- D The frequency of the signal and the length of the line

B-006-002-001 (A)

What is a coaxial cable?

- A A center wire inside an insulating material which is covered by a metal sleeve or shield
- B Two wires side-by-side in a plastic ribbon
- C Two wires side-by-side held apart by insulating rods
- D Two wires twisted around each other in a spiral

B-006-002-002 (D)

What is parallel-conductor transmission line?

- A Two wires twisted around each other in a spiral
- B A center wire inside an insulating material which is covered by a metal sleeve or shield
- C A metal pipe which is as wide or slightly wider than a wavelength of the signal it carries
- D Two wires side-by-side held apart by insulating material

B-006-002-003 (B)

What kind of antenna transmission line is made of two conductors held apart by insulated rods?

- A Twisted pair
- B Open wire line
- C Coaxial cable
- D Twin lead in a plastic ribbon

B-006-002-004 (D)

What does the term "balun" mean?

- A Balanced unloader
- B Balanced unmodulator
- C Balanced antenna network
- D Balanced to unbalanced

B-006-002-005 (A)

Where would you install a balun to feed a dipole antenna with 50-ohm coaxial cable?

- A Between the coaxial cable and the antenna
- B Between the transmitter and the coaxial cable
- C Between the antenna and the ground
- D Between the coaxial cable and the ground

B-006-002-006 (A)

What is an unbalanced line?

- A Transmission line with one conductor connected to ground
- B Transmission line with neither conductor connected to ground
- C Transmission line with both conductors connected to ground
- D Transmission line with both conductors connected to each other

B-006-002-007 (D)

What device can be installed to feed a balanced antenna with an unbalanced transmission line?

- A A triaxial transformer
- B A wave trap
- C A loading coil
- D A balun

B-006-002-008 (B)

A flexible coaxial line contains:

- A two parallel conductors separated by spacers
- B braided shield conductor and insulation around a central conductor
- C four or more conductors running parallel
- D only one conductor

B-006-002-009 (D)

A balanced transmission line:

- A has one conductor inside the other
- B carries RF current on one wire only
- C is made of one conductor only
- D is made of two parallel wires

B-006-002-010 (B)

A 75 ohm transmission line could be matched to the 300 ohm feed point of an antenna:

- A by inserting a diode in one leg of the antenna
- B by using a 4 to 1 impedance transformer
- C with an extra 250 ohm resistor
- D by using a 4 to 1 trigatron

B-006-002-011 (A)

What kind of antenna transmission line can be constructed using two conductors which are maintained a uniform distance apart using insulated spreaders?

- A 600 ohm open wire line
- B Coaxial cable
- C 75 ohm twin-lead
- D 300 ohm twin-lead

B-006-003-001 (C)

Why does coaxial cable make a good antenna transmission line?

- A It can be used near metal objects, and its impedance is higher than that of most amateur antennas
- B You can make it at home, and its impedance matches most amateur antennas
- C It is weatherproof, and its impedance matches most amateur antennas
- D It is weatherproof, and its impedance is higher than that of most amateur antennas