

B-005-006-002 (C)

How many watts of electrical power are used by a 12 volt DC light bulb that draws 0.2 ampere?

- A 24 watts
- B 6 watts
- C 2.4 watts
- D 60 watts

B-005-006-003 (C)

The DC input power of a transmitter operating at 12 volts and drawing 500 milliamperes would be:

- A 500 watts
- B 12 watts
- C 6 watts
- D 20 watts

B-005-006-004 (A)

When two 500 ohm 1 watt resistors are connected in series, the maximum total power that can be dissipated by the resistors is:

- A 2 watts
- B 1 watt
- C 1/2 watt
- D 4 watts

B-005-006-005 (C)

When two 500 ohm 1 watt resistors are connected in parallel, they can dissipate a maximum total power of:

- A 1 watt
- B 4 watts
- C 2 watts
- D 1/2 watt

B-005-006-006 (C)

If the voltage applied to two resistors in series is doubled, how much will the total power change?

- A Double
- B No change
- C Increase four times
- D Decrease to half

B-005-006-007 (D)

Which combination of resistors could make up a 50 ohms dummy load capable of safely dissipating 5 watts?

- A Two 5-watt 100 ohms resistors in series
- B Two 2-watt 25 ohms resistors in series
- C Ten quarter-watt 500 ohms resistors in parallel
- D Four 2-watt 200 ohms resistors in parallel

B-005-006-008 (A)

A 12 volt light bulb is rated at a power of 30 watts. The current drawn would be:

- A 30/12 amperes
- B 18 amperes
- C 360 amperes
- D 12/30 amperes

B-005-006-009 (B)

If two 10 ohm resistors are connected in series with a 10 volt battery, the power consumption would be:

- A 100 watts
- B 5 watts
- C 10 watts
- D 20 watts

B-005-006-010 (B)

One advantage of replacing a 50 ohm resistor with a parallel combination of two similarly rated 100 ohm resistors is that the parallel combination will have:

- A lesser resistance and similar power rating
- B the same resistance but greater power rating
- C the same resistance but lesser power rating
- D greater resistance and similar power rating

B-005-006-011 (D)

Resistor wattage ratings are:

- A calculated according to physical size and tolerance rating
- B expressed in joules
- C variable in steps of one hundred
- D determined by heat dissipation qualities

B-005-007-001 (A)

What term means the number of times per second that an alternating current flows back and forth?

- A Frequency
- B Speed
- C Pulse rate
- D Inductance

B-005-007-002 (D)

Approximately what frequency range can most humans hear?

- A 20 000 - 30 000 Hz
- B 200 - 200 000 Hz
- C 0 - 20 Hz
- D 20 - 20 000 Hz

B-005-007-003 (D)

Why do we call signals in the range 20 Hz to 20 000 Hz audio frequencies?

- A Because the human ear cannot sense anything in this range
- B Because this range is too low for radio energy
- C Because the human ear can sense radio waves in this range
- D Because the human ear can sense sounds in this range

B-005-007-004 (D)

Electrical energy at a frequency of 7125 kHz is in what frequency range?

- A Audio
- B Hyper
- C Super-high
- D Radio

B-005-007-005 (C)

What is the name for the distance an AC signal travels during one complete cycle?

- A Waveform
- B Wave spread
- C Wavelength
- D Wave speed

B-005-007-006 (D)

What happens to a signal's wavelength as its frequency increases?

- A It gets longer
- B It stays the same
- C It disappears
- D It gets shorter

B-005-007-007 (C)

What happens to a signal's frequency as its wavelength gets longer?

- A It stays the same
- B It goes up
- C It goes down
- D It disappears

B-005-007-008 (D)

What does 60 hertz (Hz) mean?

- A 6000 metres per second
- B 60 metres per second
- C 6000 cycles per second
- D 60 cycles per second

B-005-007-009 (A)

If the frequency of the waveform is 100 Hz, the time for one cycle is:

- A 0.01 second
- B 10 seconds
- C 0.0001 second
- D 1 second

B-005-007-010 (B)

Current in an AC circuit goes through a complete cycle in 0.1 second. This means the AC has a frequency of:

- A 1000 Hz
- B 10 Hz
- C 1 Hz
- D 100 Hz

B-005-007-011 (C)

A signal is composed of a fundamental frequency of 2 kHz and another of 4 kHz. This 4 kHz signal is referred to as:

- A the DC component of the main signal
- B a dielectric signal of the main signal
- C a harmonic of the 2 kHz signal
- D a fundamental of the 2 kHz signal

B-005-008-001 (A)

A two-times increase in power results in a change of how many dB?

- A 3 dB higher
- B 6 dB higher
- C 12 dB higher
- D 1 dB higher

B-005-008-002 (A)

How can you decrease your transmitter's power by 3 dB?

- A Divide the original power by 2
- B Divide the original power by 1.5
- C Divide the original power by 3
- D Divide the original power by 4

B-005-008-003 (D)

How can you increase your transmitter's power by 6 dB?

- A Multiply the original power by 3
- B Multiply the original power by 2
- C Multiply the original power by 1.5
- D Multiply the original power by 4

B-005-008-004 (B)

If a signal-strength report is "10 dB over S9", what should the report be if the transmitter power is reduced from 1500 watts to 150 watts?

- A S9 plus 5 dB
- B S9
- C S9 plus 3 dB
- D S9 minus 10 dB

B-005-008-005 (C)

If a signal-strength report is "20 dB over S9", what should the report be if the transmitter power is reduced from 1500 watts to 150 watts?

- A S9 plus 3 dB
- B S9
- C S9 plus 10 dB
- D S9 plus 5 dB

B-005-008-006 (A)

The unit "decibel" is used to indicate:

- A a mathematical ratio
- B an oscilloscope wave form
- C certain radio waves
- D a single side band signal

B-005-008-007 (A)

The power output from a transmitter increases from 1 watt to 2 watts. This is a dB increase of:

- A 3
- B 30
- C 6
- D 1

B-005-008-008 (A)

The power of a transmitter is increased from 5 watts to 50 watts by a linear amplifier. The power gain, expressed in dB, is:

- A 10 dB
- B 30 dB
- C 40 dB
- D 20 dB

B-005-008-009 (A)

You add a 9 dB gain amplifier to your 2 watt handheld. What is the power output of the combination?

- A 16 watts
- B 11 watts
- C 20 watts
- D 18 watts

B-005-008-010 (C)

The power of a transmitter is increased from 2 watts to 8 watts. This is a power gain of _____ dB.

- A 8 dB
- B 9 dB
- C 6 dB
- D 3 dB

B-005-008-011 (C)

A local amateur reports your 100W 2M simplex VHF transmission as 30 dB over S9. To reduce your signal to S9, you would reduce your power to _____ watts.

- A 10 W
- B 33.3 W
- C 100 mW
- D 1 W

B-005-009-001 (C)

If two equal-value inductors are connected in series, what is their total inductance?

- A The same as the value of either inductor
- B The value of one inductor times the value of the other
- C Twice the value of one inductor
- D Half the value of one inductor

B-005-009-002 (D)

If two equal-value inductors are connected in parallel, what is their total inductance?

- A Twice the value of one inductor
- B The same as the value of either inductor
- C The value of one inductor times the value of the other
- D Half the value of one inductor

B-005-009-003 (D)

If two equal-value capacitors are connected in series, what is their total capacitance?

- A Twice the value of one capacitor
- B The same as the value of either capacitor
- C The value of one capacitor times the value of the other
- D Half the value of either capacitor

B-005-009-004 (D)

If two equal-value capacitors are connected in parallel, what is their total capacitance?

- A The same as the value of either capacitor
- B The value of one capacitor times the value of the other
- C Half the value of one capacitor
- D Twice the value of one capacitor

B-005-009-005 (D)

What determines the inductance of a coil?

- A The core material, the number of turns used to wind the coil and the frequency of the current through the coil
- B The coil diameter, the number of turns of wire used to wind the coil and the type of metal used for the wire
- C The core material, the coil diameter, the length of the coil and whether the coil is mounted horizontally or vertically
- D The core material, the coil diameter, the length of the coil and the number of turns of wire used to wind the coil

B-005-009-006 (C)

What determines the capacitance of a capacitor?

- A The number of plates, the spacing between the plates and whether the dielectric material is N type or P type
- B The material between the plates, the area of one plate, the number of plates and the material used for the protective coating
- C The material between the plates, the surface area of the plates, the number of plates and the spacing between the plates
- D The material between the plates, the number of plates and the size of the wires connected to the plates

B-005-009-008 (B)

To replace a faulty 10 millihenry choke, you could use two:

- A 5 millihenry chokes in parallel
- B 5 millihenry chokes in series
- C 20 millihenry chokes in series
- D 30 millihenry chokes in parallel

B-005-009-009 (A)

Three 15 microfarad capacitors are wired in series. The total capacitance of this arrangement is:

- A 5 microfarads
- B 45 microfarads
- C 12 microfarads
- D 18 microfarads

B-005-009-010 (D)

Which series combinations of capacitors would best replace a faulty 10 microfarad capacitor?

- A Two 10 microfarad capacitors
- B Twenty 2 microfarad capacitors
- C Ten 2 microfarad capacitors
- D Two 20 microfarad capacitors

B-005-009-011 (D)

The total capacitance of two or more capacitors in series is:

- A found by adding each of the capacitors together and dividing by the total number of capacitors
- B found by adding each of the capacitors together
- C always greater than the largest capacitor
- D always less than the smallest capacitor

B-005-010-001 (D)

How does a coil react to AC?

- A As the amplitude of the applied AC increases, the reactance decreases
- B As the amplitude of the applied AC increases, the reactance increases
- C As the frequency of the applied AC increases, the reactance decreases
- D As the frequency of the applied AC increases, the reactance increases

B-005-010-002 (D)

How does a capacitor react to AC?

- A As the frequency of the applied AC increases, the reactance increases
- B As the amplitude of the applied AC increases, the reactance increases
- C As the amplitude of the applied AC increases, the reactance decreases
- D As the frequency of the applied AC increases, the reactance decreases

B-005-010-003 (D)

The reactance of capacitors increases as:

- A applied voltage increases
- B applied voltage decreases
- C frequency increases
- D frequency decreases

B-005-010-004 (B)

In inductances, AC may be opposed by both resistance of winding wire and reactance due to inductive effect. The term which includes resistance and reactance is:

- A capacitance
- B impedance
- C resonance
- D inductance

B-005-010-005 (B)

Capacitive reactance:

- A increases with the time constant
- B decreases as frequency increases
- C applies only to series RLC circuits
- D increases as frequency increases

B-005-010-006 (D)

Inductive reactance may be increased by:

- A a decrease in the applied frequency
- B a decrease in the supplied current
- C an increase in the applied voltage
- D an increase in the applied frequency

B-005-010-007 (C)

What property allows a coil wound on a ferrite core to mitigate the effects of an offending radio signal?

- A Low reactance at audio frequencies
- B High reactance at audio frequencies
- C High reactance at radio frequencies
- D Low reactance at radio frequencies

B-005-010-008 (A)

What property allows an RF bypass capacitor on an audio circuit to divert an offending radio signal?

- A Low reactance at radio frequencies
- B High reactance at radio frequencies
- C Low reactance at audio frequencies
- D High reactance at audio frequencies

B-005-010-009 (A)

What property allows an RF bypass capacitor to have little effect on an audio circuit?

- A High reactance at low frequencies
- B Low reactance at high frequencies
- C High reactance at high frequencies
- D Low reactance at low frequencies

B-005-010-010 (D)

What property allows an RF choke coil to have little effect on signals meant to flow through the coil?

- A High reactance at low frequencies
- B Low reactance at high frequencies
- C High reactance at high frequencies
- D Low reactance at low frequencies

B-005-010-011 (D)

In general, the reactance of inductors increases with:

- A decreasing AC frequency
- B decreasing applied voltage
- C increasing applied voltage
- D increasing AC frequency

B-005-011-001 (D)

If no load is attached to the secondary winding of a transformer, what is current in the primary winding called?

- A Direct current
- B Latent current
- C Stabilizing current
- D Magnetizing current

B-005-011-002 (B)

A transformer operates a 6.3 volt 2 ampere light bulb from its secondary winding. The input power to the primary winding is approximately:

- A 3 watts
- B 13 watts
- C 6 watts
- D 8 watts

B-005-011-003 (B)

A transformer has a 240 volt primary that draws a current of 250 milliamperes from the mains supply. Assuming no losses and only one secondary, what current would be available from the 12 volt secondary?

- A 50 amperes
- B 5 amperes
- C 215 amperes
- D 25 amperes

B-005-011-004 (C)

In a mains power transformer, the primary winding has 250 turns, and the secondary has 500. If the input voltage is 120 volts, the likely secondary voltage is:

- A 610 V
- B 26 V
- C 240 V
- D 480 V

B-005-011-005 (B)

The strength of the magnetic field around a conductor in air is:

- A inversely proportional to the voltage on the conductor
- B directly proportional to the current in the conductor
- C inversely proportional to the diameter of the conductor
- D directly proportional to the diameter of the conductor

B-005-011-006 (A)

Maximum induced voltage in a coil occurs when:

- A current is going through its greatest rate of change
- B the current through the coil is of a DC nature
- C current is going through its least rate of change
- D the magnetic field around the coil is not changing