

A-001-001-001 (C)

What is the meaning of the term "time constant" in an RL circuit ?

- A The time required for the voltage in the circuit to build up to 63.2% of the maximum value
- B The time required for the voltage in the circuit to build up to 36.8% of the maximum value
- C The time required for the current in the circuit to build up to 63.2% of the maximum value
- D The time required for the current in the circuit to build up to 36.8% of the maximum value

A-001-001-002 (B)

What is the term for the time required for the capacitor in an RC circuit to be charged to 63.2% of the supply voltage?

- A One exponential period
- B One time constant
- C An exponential rate of one
- D A time factor of one

A-001-001-003 (C)

What is the term for the time required for the current in an RL circuit to build up to 63.2% of the maximum value?

- A A time factor of one
- B One exponential rate
- C One time constant
- D An exponential period of one

A-001-001-004 (B)

What is the term for the time it takes for a charged capacitor in an RC circuit to discharge to 36.8% of its initial value of stored charge?

- A One discharge period
- B One time constant
- C A discharge factor of one
- D An exponential discharge of one

A-001-001-005 (A)

What is meant by "back EMF"?

- A A voltage that opposes the applied EMF
- B A current that opposes the applied EMF
- C An opposing EMF equal to R times C percent of the applied EMF
- D A current equal to the applied EMF

A-001-001-006 (B)

After two time constants, the capacitor in an RC circuit is charged to what percentage of the supply voltage?

- A 36.8%
- B 86.5%
- C 63.2%
- D 95%

A-001-001-007 (B)

After two time constants, the capacitor in an RC circuit is discharged to what percentage of the starting voltage?

- A 63.2%
- B 13.5%
- C 36.8%
- D 86.5%

A-001-001-008 (D)

What is the time constant of a circuit having a 100 microfarad capacitor in series with a 470 kilohm resistor?

- A 4700 seconds
- B 470 seconds
- C 0.47 seconds
- D 47 seconds

A-001-001-009 (B)

What is the time constant of a circuit having a 470 microfarad capacitor in series with a 470 kilohm resistor?

- A 470 seconds
- B 221 seconds
- C 221 000 seconds
- D 47 000 seconds

A-001-001-010 (D)

What is the time constant of a circuit having a 220 microfarad capacitor in series with a 470 kilohm resistor?

- A 470 000 seconds
- B 470 seconds
- C 220 seconds
- D 103 seconds

A-001-002-001 (A)

What is the result of skin effect?

- A As frequency increases, RF current flows in a thinner layer of the conductor, closer to the surface
- B As frequency decreases, RF current flows in a thinner layer of the conductor, closer to the surface
- C Thermal effects on the surface of the conductor increase impedance
- D Thermal effects on the surface of the conductor decrease impedance

A-001-002-002 (B)

What effect causes most of an RF current to flow along the surface of a conductor?

- A Layer effect
- B Skin effect
- C Piezoelectric effect
- D Resonance effect

A-001-002-003 (B)

Where does almost all RF current flow in a conductor?

- A In the centre of the conductor
- B Along the surface of the conductor
- C In a magnetic field in the centre of the conductor
- D In a magnetic field around the conductor

A-001-002-004 (B)

Why does most of an RF current flow within a very thin layer under the conductor's surface?

- A Because of heating of the conductor's interior
- B Because of skin effect
- C Because the RF resistance of a conductor is much less than the DC resistance
- D Because a conductor has AC resistance due to self-inductance

A-001-002-005 (B)

Why is the resistance of a conductor different for RF currents than for direct currents?

- A Because the insulation conducts current at high frequencies
- B Because of skin effect
- C Because of the Hertzberg effect
- D Because conductors are non-linear devices

A-001-002-006 (A)

What unit measures the ability of a capacitor to store electrical charge?

- A Farad
- B Coulomb
- C Watt
- D Volt

A-001-002-007 (B)

A wire has a current passing through it. Surrounding this wire there is:

- A a skin effect that diminishes with distance
- B an electromagnetic field
- C an electrostatic field
- D a cloud of electrons

A-001-002-008 (A)

In what direction is the magnetic field oriented about a conductor in relation to the direction of electron flow?

- A In the direction determined by the left-hand rule
- B In all directions
- C In the same direction as the current
- D In the direct opposite to the current

A-001-002-009 (D)

What is the term for energy that is stored in an electromagnetic or electrostatic field?

- A Kinetic energy
- B Ampere-joules
- C Joule-coulombs
- D Potential energy

A-001-002-010 (D)

Between the charged plates of a capacitor there is:

- A a magnetic field
- B a cloud of electrons
- C an electric current
- D an electrostatic field

A-001-002-011 (C)

Energy is stored within an inductor that is carrying a current. The amount of energy depends on this current, but it also depends on a property of the inductor. This property has the following unit:

- A farad
- B watt
- C henry
- D coulomb

A-001-003-001 (C)

What is the resonant frequency of a series RLC circuit if R is 47 ohms, L is 50 microhenrys and C is 40 picofarads?

- A 7.96 MHz
- B 79.6 MHz
- C 3.56 MHz
- D 1.78 MHz

A-001-003-002 (D)

What is the resonant frequency of a series RLC circuit, if R is 47 ohms, L is 40 microhenrys and C is 200 picofarads?

- A 1.99 kHz
- B 1.99 MHz
- C 1.78 kHz
- D 1.78 MHz

A-001-003-003 (D)

What is the resonant frequency of a series RLC circuit, if R is 47 ohms, L is 50 microhenrys and C is 10 picofarads?

- A 7.12 kHz
- B 3.18 MHz
- C 3.18 kHz
- D 7.12 MHz

A-001-003-004 (A)

What is the resonant frequency of a series RLC circuit, if R is 47 ohms, L is 25 microhenrys and C is 10 picofarads?

- A 10.1 MHz
- B 63.7 MHz
- C 10.1 kHz
- D 63.7 kHz

A-001-003-005 (A)

What is the resonant frequency of a series RLC circuit, if R is 47 ohms, L is 3 microhenrys and C is 40 picofarads?

- A 14.5 MHz
- B 13.1 MHz
- C 13.1 kHz
- D 14.5 kHz

A-001-003-006 (C)

What is the resonant frequency of a series RLC circuit, if R is 47 ohms, L is 4 microhenrys and C is 20 picofarads?

- A 19.9 kHz
- B 17.8 kHz
- C 17.8 MHz
- D 19.9 MHz

A-001-003-007 (B)

What is the resonant frequency of a series RLC circuit, if R is 47 ohms, L is 8 microhenrys and C is 7 picofarads?

- A 2.13 MHz
- B 21.3 MHz
- C 28.4 MHz
- D 2.84 MHz

A-001-003-008 (C)

What is the resonant frequency of a series RLC circuit, if R is 47 ohms, L is 3 microhenrys and C is 15 picofarads?

- A 35.4 kHz
- B 23.7 kHz
- C 23.7 MHz
- D 35.4 MHz

A-001-003-009 (C)

What is the resonant frequency of a series RLC circuit, if R is 47 ohms, L is 4 microhenrys and C is 8 picofarads?

- A 49.7 kHz
- B 28.1 kHz
- C 28.1 MHz
- D 49.7 MHz

A-001-003-010 (B)

What is the resonant frequency of a series RLC circuit, if R is 47 ohms, L is 1 microhenry and C is 9 picofarads?

- A 1.77 MHz
- B 53.1 MHz
- C 5.31 MHz
- D 17.7 MHz

A-001-003-011 (A)

What is the value of capacitance (C) in a series R-L-C circuit, if the circuit resonant frequency is 14.25 MHz and L is 2.84 microhenrys?

- A 44 picofarads
- B 2.2 microfarads
- C 44 microfarads
- D 2.2 picofarads

A-001-004-001 (D)

What is the resonant frequency of a parallel RLC circuit if R is 4.7 kilohms, L is 1 microhenry and C is 10 picofarads?

- A 15.9 kHz
- B 50.3 kHz
- C 15.9 MHz
- D 50.3 MHz

A-001-004-002 (D)

What is the resonant frequency of a parallel RLC circuit if R is 4.7 kilohms, L is 2 microhenrys and C is 15 picofarads?

- A 29.1 kHz
- B 5.31 MHz
- C 5.31 kHz
- D 29.1 MHz

A-001-004-003 (C)

What is the resonant frequency of a parallel RLC circuit if R is 4.7 kilohms, L is 5 microhenrys and C is 9 picofarads?

- A 3.54 MHz
- B 3.54 kHz
- C 23.7 MHz
- D 23.7 kHz

A-001-004-004 (B)

What is the resonant frequency of a parallel RLC circuit if R is 4.7 kilohms, L is 2 microhenrys and C is 30 picofarads?

- A 20.5 kHz
- B 20.5 MHz
- C 2.65 MHz
- D 2.65 kHz

A-001-004-005 (A)

What is the resonant frequency of a parallel RLC circuit if R is 4.7 kilohms, L is 15 microhenrys and C is 5 picofarads?

- A 18.4 MHz
- B 2.12 kHz
- C 2.12 MHz
- D 18.4 kHz

A-001-004-006 (D)

What is the resonant frequency of a parallel RLC circuit if R is 4.7 kilohms, L is 3 microhenrys and C is 40 picofarads?

- A 1.33 kHz
- B 1.33 MHz
- C 14.5 kHz
- D 14.5 MHz

A-001-004-007 (A)

What is the resonant frequency of a parallel RLC circuit if R is 4.7 kilohms, L is 40 microhenrys and C is 6 picofarads?

- A 10.3 MHz
- B 6.63 MHz
- C 6.63 kHz
- D 10.3 kHz

A-001-004-008 (D)

What is the resonant frequency of a parallel RLC circuit if R is 4.7 kilohms, L is 10 microhenrys and C is 50 picofarads?

- A 7.12 kHz
- B 3.18 MHz
- C 3.18 kHz
- D 7.12 MHz

A-001-004-009 (D)

What is the resonant frequency of a parallel RLC circuit if R is 4.7 kilohms, L is 200 microhenrys and C is 10 picofarads?

- A 3.56 kHz
- B 7.96 MHz
- C 7.96 kHz
- D 3.56 MHz

A-001-004-010 (D)

What is the resonant frequency of a parallel RLC circuit if R is 4.7 kilohms, L is 90 microhenrys and C is 100 picofarads?

- A 1.77 kHz
- B 1.77 MHz
- C 1.68 kHz
- D 1.68 MHz

A-001-004-011 (C)

What is the value of inductance (L) in a parallel RLC circuit, if the resonant frequency is 14.25 MHz and C is 44 picofarads?

- A 3.9 millihenrys
- B 0.353 microhenry
- C 2.8 microhenrys
- D 253.8 millihenrys

A-001-005-001 (D)

What is the Q of a parallel RLC circuit, if it is resonant at 14.128 MHz, L is 2.7 microhenrys and R is 18 kilohms?

- A 7.51
- B 0.013
- C 71.5
- D 75.1

A-001-005-002 (B)

What is the Q of a parallel RLC circuit, if it is resonant at 14.128 MHz, L is 4.7 microhenrys and R is 18 kilohms?

- A 4.31
- B 43.1
- C 13.3
- D 0.023

A-001-005-003 (B)

What is the Q of a parallel RLC circuit, if it is resonant at 4.468 MHz, L is 47 microhenrys and R is 180 ohms?

- A 13.3
- B 0.136
- C 7.35
- D 0.00735

A-001-005-004 (B)

What is the Q of a parallel RLC circuit, if it is resonant at 14.225 MHz, L is 3.5 microhenrys and R is 10 kilohms?

- A 71.5
- B 31.9
- C 7.35
- D 0.0319

A-001-005-005 (B)

What is the Q of a parallel RLC circuit, if it is resonant at 7.125 MHz, L is 8.2 microhenrys and R is 1 kilohm?

- A 0.273
- B 2.73
- C 36.8
- D 0.368

A-001-005-006 (A)

What is the Q of a parallel RLC circuit, if it is resonant at 7.125 MHz, L is 10.1 microhenrys and R is 100 ohms?

- A 0.221
- B 22.1
- C 0.00452
- D 4.52

A-001-005-007 (A)

What is the Q of a parallel RLC circuit, if it is resonant at 7.125 MHz, L is 12.6 microhenrys and R is 22 kilohms?

- A 39
- B 22.1
- C 0.0256
- D 25.6

A-001-005-008 (D)

What is the Q of a parallel RLC circuit, if it is resonant at 3.625 MHz, L is 3 microhenrys and R is 2.2 kilohms?

- A 25.6
- B 31.1
- C 0.031
- D 32.2

A-001-005-009 (C)

What is the Q of a parallel RLC circuit, if it is resonant at 3.625 MHz, L is 42 microhenrys and R is 220 ohms?

- A 4.35
- B 0.00435
- C 0.23
- D 2.3

A-001-005-010 (C)

What is the Q of a parallel RLC circuit, if it is resonant at 3.625 MHz, L is 43 microhenrys and R is 1.8 kilohms?

- A 54.3
- B 23
- C 1.84
- D 0.543

A-001-005-011 (A)

Why is a resistor often included in a parallel resonant circuit ?

- A To decrease the Q and increase the bandwidth
- B To increase the Q and decrease the skin effect
- C To decrease the Q and increase the resonant frequency
- D To increase the Q and decrease bandwidth

A-002-001-001 (D)

What two elements widely used in semiconductor devices exhibit both metallic and non-metallic characteristics?

- A Galena and germanium
- B Galena and bismuth
- C Silicon and gold
- D Silicon and germanium

A-002-001-002 (C)

In what application is gallium-arsenide used as a semiconductor material in preference to germanium or silicon?

- A At very low frequencies
- B In bipolar transistors
- C At microwave frequencies
- D In high-power circuits

A-002-001-003 (C)

What type of semiconductor material contains fewer free electrons than pure germanium or silicon crystals?

- A Bipolar type
- B Superconductor type
- C P-type
- D N-type

A-002-001-004 (A)

What type of semiconductor material contains more free electrons than pure germanium or silicon crystals?

- A N-type
- B P-type
- C Bipolar
- D Superconductor