B-003-002-001 (A)

In a frequency modulation transmitter, the input to the speech amplifier is connected to the:

- A microphone
- B modulator
- C power amplifier
- D frequency multiplier

B-003-002-002 (C)

In a frequency modulation transmitter, the microphone is connected to the:

- A power amplifier
- B oscillator
- C speech amplifier
- D modulator

B-003-002-003 (C)

In a frequency modulation transmitter, the _____is in between the speech amplifier and the oscillator.

- A microphone
- B frequency multiplier
- C modulator
- D power amplifier

B-003-002-004 (A)

In a frequency modulation transmitter, the ______is located between the modulator and the frequency multiplier.

- A oscillator
- B speech amplifier
- C power amplifier
- D microphone

B-003-002-005 (A)

In a frequency modulation transmitter, the ______is located between the oscillator and the power amplifier.

- A frequency multiplier
- **B** microphone
- C speech amplifier
- D modulator

B-003-002-006 (D)

In a frequency modulation transmitter, the _____ is located between the frequency multiplier and the antenna.

- A modulator
- B speech amplifier
- C oscillator
- D power amplifier

B-003-002-007 (A)

In a frequency modulation transmitter, the power amplifier output is connected to the:

- A antenna
- B frequency multiplier
- C microphone
- D modulator

B-003-003-001 (A)

In a frequency modulation receiver, the _____is connected to the input of the radio frequency amplifier.

- A antenna
- B mixer
- C frequency discriminator
- D limiter

B-003-003-002 (C)

In a frequency modulation receiver, the _____ is in between the antenna and the mixer.

- A local oscillator
- B intermediate frequency amplifier
- C radio frequency amplifier
- D audio frequency amplifier

B-003-003-003 (A)

In a frequency modulation receiver, the output of the local oscillator is fed to the:

- A mixer
- B radio frequency amplifier
- C limiter
- D antenna

B-003-003-004 (D)	B-003-003-009 (D)
In a frequency modulation receiver, the output of theis connected to the mixer.	In a frequency modulation receiver, the is located between the speaker or headphones and the frequency
A frequency discriminator	discriminator.
B intermediate frequency amplifier	A limiter
C speaker or headphones	B intermediate frequency amplifier
D local oscillator	C radio frequency amplifier
	D audio frequency amplifier
B-003-003-005 (D)	
In a frequency modulation receiver,	B-003-003-010 (C)
the is in between the mixer and	In a frequency modulation receiver, the
the intermediate frequency amplifier.	connects to the audio frequency amplifier output.
A limiter	
B frequency discriminator	A frequency discriminator
C radio frequency amplifier	B limiter
D filter	C speaker or headphones
	D intermediate frequency amplifier
B-003-003-006 (C)	B-003-004-001 (B)
In a frequency modulation receiver, the	` '
the limiter.	In a CW transmitter, the output from the is connected to the driver/buffer.
A mixer	A power supply
B radio frequency amplifier	B master oscillator
C intermediate frequency amplifier	C power amplifier
D local oscillator	D telegraph key
B-003-003-007 (A)	B-003-004-002 (C)
In a frequency modulation receiver,	In a typical CW transmitter, the
the is in between the intermediate frequency amplifier and the	is the primary source of direct current.
frequency discriminator.	
A limiter	A power amplifier
B filter	B master oscillator
C local oscillator	C power supply
D radio frequency amplifier	D driver/buffer
- Tadio iroquorioy ampinior	B-003-004-003 (B)
B-003-003-008 (A)	, ,
In a frequency modulation receiver, the	In a CW transmitter, the is between the master oscillator and the power
is located between the limiter	amplifier.
and the audio frequency amplifier.	A telegraph key
A frequency discriminator	B driver/buffer
B intermediate frequency amplifier	C audio amplifier
C speaker or headphones	D power supply
D local oscillator	· · · · ·

B-003-004-004 (A)	B-003-005-003 (A)
In a CW transmitter, the controls when RF energy is applied to the antenna.	In a single sideband and CW receiver, the is connected to the radio frequency amplifier and the local oscillator.
A telegraph key	A mixer
B master oscillator	B beat frequency oscillator
C driver/buffer	C product detector
D power amplifier	D filter
B-003-004-005 (D)	B-003-005-004 (B)
In a CW transmitter, the is in between the driver/buffer stage and the antenna.	In a single sideband and CW receiver, the output of the is connected to the mixer.
A power supply	A product detector
B telegraph key	B local oscillator
C master oscillator	C intermediate frequency amplifier
D power amplifier	D beat frequency oscillator
B-003-004-006 (A)	B-003-005-005 (C)
In a CW transmitter, the output of the is transferred to the	In a single sideband and CW receiver, the is in between the mixer and
antenna.	intermediate frequency amplifier.
A power amplifier	A beat frequency oscillator
B driver/buffer	B product detector
C power supply	C filter
D master oscillator	D radio frequency amplifier
B-003-005-001 (D)	B-003-005-006 (D)
In a single sideband and CW receiver, the antenna is connected to the	In a single sideband and CW receiver, the is in between the filter and
A product detector	product detector.
B local oscillator	A audio frequency amplifier
C intermediate frequency amplifier	B beat frequency oscillator
D radio frequency amplifier	C radio frequency amplifier
	D intermediate frequency amplifier
B-003-005-002 (D)	D 000 005 007 (B)
In a single sideband and CW receiver, the	B-003-005-007 (D)
output of the is connected to the mixer.	In a single sideband and CW receiver, the output is connected to the
A filter	audio frequency amplifier.
B intermediate frequency amplifier	A local oscillator
C audio frequency amplifier	B beat frequency oscillator
D radio frequency amplifier	C intermediate frequency amplifier
	D product detector

B-003-005-008 (D)	B-003-006-003 (B)
In a single sideband and CW receiver, the output of the is connected to the product detector.	In a single sideband transmitter, the is in between the balanced modulator and the mixer.
A mixer	A microphone
B radio frequency amplifier	B filter
C audio frequency amplifier	C radio frequency oscillator
D beat frequency oscillator	D speech amplifier
B-003-005-009 (C)	B-003-006-004 (A)
In a single sideband and CW receiver, the is connected to the output of the product detector.	In a single sideband transmitter, the is connected to the speech amplifier.
A local oscillator	A microphone
B radio frequency amplifier	B radio frequency oscillator
C audio frequency amplifier	C filter
D intermediate frequency amplifier	D mixer
B-003-005-010 (D)	B-003-006-005 (C)
In a single sideband and CW receiver, the is connected to the output of the audio frequency amplifier.	In a single sideband transmitter, the output of the is connected to the balanced modulator.
A mixer	A variable frequency oscillator
B radio frequency amplifier	B linear amplifier
C beat frequency oscillator	C speech amplifier
D speaker or headphones	D filter
D 000 000 004 (D)	D 000 000 000 (D)
B-003-006-001 (B)	B-003-006-006 (D)
In a single sideband transmitter, the output of the is connected to the balanced modulator.	In a single sideband transmitter, the output of the variable frequency oscillator is connected to the
A mixer	A antenna
B radio frequency oscillator	B balanced modulator
C variable frequency oscillator	C linear amplifier
D linear amplifier	D mixer
B-003-006-002 (B)	B-003-006-007 (A)
In a single sideband transmitter, the output of the is connected to the filter.	In a single sideband transmitter, the output of the is connected to the mixer
	A variable frequency oscillator
A radio frequency oscillator	B radio frequency oscillator
B balanced modulator	C linear amplifier
C microphone D mixer	D antenna
¬ ΠΙΙ Υ ΦΙ	

B-003-006-008 (D)	B-003-007-004 (A)
In an single sideband transmitter, the is in between the mixer and the antenna.	In an amateur digital radio system, the audio connections of the modem/sound card are connected to the
A variable frequency oscillator	
B balanced modulator	B input/output
c radio frequency oscillatorD linear amplifier	C scanner D antenna
ilitear amplifier	D antenna
B-003-006-009 (C)	B-003-007-005 (C)
In a single sideband transmitter, the output	In an amateur digital radio system, the
of the linear amplifier is connected to the	modem function is often performed by the
·	computer
A variable frequency oscillator	A scanner
B speech amplifier	B serial port
C antenna	C sound card
D filter	D keyboard
B-003-007-001 (C)	B-003-008-001 (D)
In an amateur digital radio system, the	In a regulated power supply, the transformer
interfaces with the	connects to an external source which is
computer.	referred to as
A power supply	A regulator
B transceiver	B filter
C input/output	C rectifier
D antenna	D input
B-003-007-002 (D)	B-003-008-002 (D)
In an amateur digital radio system, the	In a regulated power supply, the
modem is connected to the	is between the input and
A amplifier	the rectifier.
B antenna	A output
C input/output	B regulator
D computer	C filter
·	D transformer
B-003-007-003 (D)	
In an amateur digital radio system, the	B-003-008-003 (B)
transceiver is connected to the	In a regulated power supply, the
·	is between the transformer and the filter.
A computer	
B scanner	A regulator
C input/output	B rectifier
D modem	C input D output
	17 (111111111

B-003-008-004 (B)

In a regulated power supply, the output of the rectifier is connected to the

- A regulator
- B filter
- C output
- D transformer

B-003-008-005 (A)

In a regulated power supply, the output of the filter connects to the

- A regulator
- **B** transformer
- C rectifier
- D output

B-003-008-006 **(D)**

In a regulated power supply, the _____is connected to the regulator.

- A rectifier
- B input
- C transformer
- \mathbb{D} output

B-003-009-001 (B)

In a Yagi 3 element directional antenna, the _____ is primarily for mechanical support purposes.

- A director
- B boom
- C reflector
- D driven element

B-003-009-002 (D)

In a Yagi 3 element directional antenna, the is the longest radiating element.

- A director
- B driven element
- C boom
- D reflector

B-003-009-003 (B)

In a Yagi 3 element directional antenna, the _____ is the shortest radiating element.

- A driven element
- B director
- C boom
- D reflector

B-003-009-004 (D)

In a Yagi 3 element directional antenna, the _____is not the longest nor the shortest radiating element.

- A boom
- B director
- C reflector
- D driven element

B-003-010-001 **(D)**

Which list of emission types is in order from the narrowest bandwidth to the widest bandwidth?

- A CW, SSB voice, RTTY, FM voice
- B CW, FM voice, RTTY, SSB voice
- C RTTY, CW, SSB voice, FM voice
- D CW, RTTY, SSB voice, FM voice

B-003-010-002 (A)

The figure in a receiver's specifications which indicates its sensitivity is the:

- A RF input signal needed to achieve a given signal plus noise to noise ratio
- B audio output in watts
- C bandwidth of the IF in kilohertz
- D number of RF amplifiers

B-003-010-003 (B)

If two receivers of different sensitivity are compared, the less sensitive receiver will produce:

- A more signal or less noise
- B less signal or more noise
- C a steady oscillator drift
- D more than one signal