

A-003-006-005 (D)

Voltmeter sensitivity is usually expressed in ohms per volt. This means that a voltmeter with a sensitivity of 20 kilohms per volt would be a:

- A 1 milliamperere meter
- B 50 milliamperere meter
- C 100 milliamperere meter
- D 50 microampere meter

A-003-006-006 (D)

The sensitivity of a voltmeter, whose resistance is 150 000 ohms on the 150-volt range, is:

- A 100 000 ohms per volt
- B 10 000 ohms per volt
- C 150 ohms per volt
- D 1000 ohms per volt

A-003-006-007 (C)

The range of a DC ammeter can easily be extended by:

- A changing the internal inductance of the meter
- B changing the internal capacitance of the meter to resonance
- C connecting an external resistance in parallel with the internal resistance
- D connecting an external resistance in series with the internal resistance

A-003-006-008 (C)

What happens inside a multimeter when you switch it from a lower to a higher voltage range?

- A Resistance is reduced in parallel with the meter
- B Resistance is added in parallel with the meter
- C Resistance is added in series with the meter
- D Resistance is reduced in series with the meter

A-003-006-009 (D)

How can the range of an ammeter be increased?

- A By adding resistance in series with the circuit under test
- B By adding resistance in parallel with the circuit under test
- C By adding resistance in series with the meter
- D By adding resistance in parallel with the meter

A-003-006-010 (B)

Where should an RF wattmeter be connected for the most accurate readings of transmitter output power?

- A At the antenna feed point
- B At the transmitter output connector
- C One-half wavelength from the transmitter output
- D One-half wavelength from the antenna feed point

A-003-006-011 (C)

At what line impedance do most RF wattmeters usually operate?

- A 100 ohms
- B 300 ohms
- C 50 ohms
- D 25 ohms

A-004-001-001 (D)

For the same transformer secondary voltage, which rectifier has the highest average output voltage?

- A Half-wave
- B Quarter-wave
- C Full-wave centre-tap
- D Bridge

A-004-001-002 (A)

In a half-wave power supply with a capacitor input filter and a load drawing little or no current, the peak inverse voltage (PIV) across the diode can reach _____ times the RMS voltage.

- A 2.8
- B 0.45
- C 5.6
- D 1.4

A-004-001-003 (D)

In a full-wave centre-tap power supply, regardless of load conditions, the peak inverse voltage (PIV) will be _____ times the RMS voltage:

- A 0.636
- B 0.707
- C 1.4
- D 2.8

A-004-001-004 (B)

A full-wave bridge rectifier circuit makes use of both halves of the AC cycle, but unlike the full-wave centre-tap rectifier circuit it does not require:

- A diodes across each leg of the transformer
- B a centre-tapped secondary on the transformer
- C any output filtering
- D a centre-tapped primary on the transformer

A-004-001-005 (B)

For a given transformer the maximum output voltage available from a full-wave bridge rectifier circuit will be:

- A the same as the half-wave rectifier
- B double that of the full-wave centre-tap rectifier
- C half that of the full-wave centre-tap rectifier
- D the same as the full-wave centre-tap rectifier

A-004-001-006 (D)

The ripple frequency produced by a full-wave power supply connected to a normal household circuit is:

- A 60 Hz
- B 90 Hz
- C 30 Hz
- D 120 Hz

A-004-001-007 (D)

The ripple frequency produced by a half-wave power supply connected to a normal household circuit is:

- A 90 Hz
- B 120 Hz
- C 30 Hz
- D 60 Hz

A-004-001-008 (D)

Full-wave voltage doublers:

- A create four times the output voltage of half-wave doublers
- B use less power than half-wave doublers
- C are used only in high-frequency power supplies
- D use both halves of an AC wave

A-004-001-009 (D)

What are the two major ratings that must not be exceeded for silicon-diode rectifiers used in power-supply circuits?

- A Average power; average voltage
- B Capacitive reactance; avalanche voltage
- C Peak load impedance; peak voltage
- D Peak inverse voltage; average forward current

A-004-001-010 (C)

In a high voltage power supply, why should a resistor and capacitor be wired in parallel with the power-supply rectifier diodes?

- A To decrease the output voltage
- B To ensure that the current through each diode is about the same
- C To equalize voltage drops and guard against transient voltage spikes
- D To smooth the output waveform

A-004-001-011 (A)

What is the output waveform of an unfiltered full-wave rectifier connected to a resistive load?

- A A series of pulses at twice the frequency of the AC input
- B A steady DC voltage
- C A sine wave at half the frequency of the AC input
- D A series of pulses at the same frequency as the AC input

A-004-002-001 (C)

Filter chokes are rated according to:

- A power loss
- B breakdown voltage
- C inductance and current-handling capacity
- D reactance at 1000 Hz

A-004-002-002 (A)

Which of the following circuits gives the best regulation, under similar load conditions?

- A A full-wave rectifier with a choke input filter
- B A half-wave bridge rectifier with a capacitor input filter
- C A half-wave rectifier with a choke input filter
- D A full-wave rectifier with a capacitor input filter

A-004-002-003 (C)

The advantage of the capacitor input filter over the choke input filter is:

- A improved voltage regulation
- B lower peak rectifier currents
- C a higher terminal voltage output
- D better filtering action or smaller ripple voltage

A-004-002-004 (C)

With a normal load, the choke input filter will give the:

- A greatest ripple frequency
- B highest output voltage
- C best regulated output
- D greatest percentage of ripple

A-004-002-005 (C)

There are two types of filters in general use in a power supply. They are called:

- A choke input and capacitor output
- B choke output and capacitor input
- C choke input and capacitor input
- D choke output and capacitor output

A-004-002-006 (A)

The main function of the bleeder resistor in a power supply is to provide a discharge path for the capacitor in the power supply. But it may also be used for a secondary function, which is to:

- A improve voltage regulation
- B provide a ground return for the transformer
- C inhibit the flow of current through the supply
- D act as a secondary smoothing device in conjunction with the filter

A-004-002-007 (C)

In a power supply, series chokes will:

- A impede the passage of DC but will pass the AC component
- B impede both DC and AC
- C readily pass the DC but will impede the flow of the AC component
- D readily pass the DC and the AC component

A-004-002-008 (D)

When using a choke input filter, a minimum current should be drawn all the time when the device is switched on. This can be accomplished by:

- A utilizing a full-wave bridge rectifier circuit
- B placing an ammeter in the output circuit
- C increasing the value of the output capacitor
- D including a suitable bleeder resistance

A-004-002-009 (D)

In the design of a power supply, the designer must be careful of resonance effects because the ripple voltage could build up to a high value. The components that must be carefully selected are:

- A the bleeder resistor and the first choke
- B first capacitor and second capacitor
- C first choke and second capacitor
- D first choke and first capacitor

A-004-002-010 (C)

Excessive rectifier peak current and abnormally high peak inverse voltages can be caused in a power supply by the filter forming a:

- A parallel resonant circuit with the first choke and second capacitor
- B tuned inductance in the filter choke
- C series resonant circuit with the first choke and first capacitor
- D short circuit across the bleeder

A-004-002-011 (A)

In a properly designed choke input filter power supply, the no-load voltage across the filter capacitor will be about nine-tenths of the AC RMS voltage; yet it is advisable to use capacitors rated at the peak transformer voltage. Why is this large safety margin suggested?

- A Under no-load conditions and a burned-out bleeder, voltages could reach the peak transformer voltage
- B Resonance can be set up in the filter producing high voltages
- C Under heavy load, high currents and voltages are produced
- D Under no-load conditions, the current could reach a high level

A-004-003-001 (A)

What is one characteristic of a linear electronic voltage regulator?

- A The conduction of a control element is varied in direct proportion to the line voltage or load current
- B It has a ramp voltage at its output
- C A pass transistor switches from its "on" state to its "off" state
- D The control device is switched on or off, with the duty cycle proportional to the line or load conditions

A-004-003-002 (D)

What is one characteristic of a switching voltage regulator?

- A The conduction of a control element is varied in direct proportion to the line voltage or load current
- B It provides more than one output voltage
- C It gives a ramp voltage at its output
- D The control device is switched on and off, with the duty cycle proportional to the line or load conditions

A-004-003-003 (D)

What device is typically used as a stable reference voltage in a linear voltage regulator?

- A An SCR
- B A varactor diode
- C A junction diode
- D A Zener diode

A-004-003-004 (C)

What type of linear regulator is used in applications requiring efficient utilization of the primary power source?

- A A constant current source
- B A shunt current source
- C A series regulator
- D A shunt regulator

A-004-003-005 (A)

What type of linear voltage regulator is used in applications requiring a constant load on the unregulated voltage source?

- A A shunt regulator
- B A constant current source
- C A shunt current source
- D A series regulator

A-004-003-006 (D)

How is remote sensing accomplished in a linear voltage regulator?

- A An error amplifier compares the input voltage to the reference voltage
- B A load connection is made outside the feedback loop
- C By wireless inductive loops
- D A feedback connection to an error amplifier is made directly to the load

A-004-003-007 (D)

What is a three-terminal regulator?

- A A regulator that supplies three voltages at a constant current
- B A regulator containing three error amplifiers and sensing transistors
- C A regulator that supplies three voltages with variable current
- D A regulator containing a voltage reference, error amplifier, sensing resistors and transistors, and a pass element

A-004-003-008 (A)

In addition to an input voltage range what are the important characteristics of a three-terminal regulator?

- A Output voltage and maximum output current
- B Maximum output voltage and minimum output current
- C Minimum output voltage and maximum output current
- D Output voltage and minimum output current

A-004-003-009 (B)

What type of voltage regulator contains a voltage reference, error amplifier, sensing resistors and transistors, and a pass element in one package?

- A A Zener regulator
- B A three-terminal regulator
- C An op-amp regulator
- D A switching regulator

A-004-003-010 (C)

When extremely low ripple is required, or when the voltage supplied to the load must remain constant under conditions of large fluctuations of current and line voltage, a closed-loop amplifier is used to regulate the power supply. There are two main categories of electronic regulators. They are:

- A linear and non-linear
- B stiff and switching
- C linear and switching
- D non-linear and switching

A-004-003-011 (C)

A modern type of regulator, which features a reference, high-gain amplifier, temperature-compensated voltage sensing resistors and transistors as well as a pass element is commonly referred to as a:

- A twenty-four pin terminal regulator
- B six-terminal regulator
- C three-terminal regulator
- D nine-pin terminal regulator

A-004-004-001 (A)

In a series-regulated power supply, the power dissipation of the pass transistor is:

- A directly proportional to the load current and the input/output voltage differential
- B the inverse of the load current and the input/output voltage differential
- C dependent upon the peak inverse voltage appearing across the Zener diode
- D indirectly proportional to the load voltage and the input/output voltage differential

A-004-004-002 (C)

In any regulated power supply, the output is cleanest and the regulation is best:

- A across the load
- B at the output of the pass transistor
- C at the point where the sampling network or error amplifier is connected
- D across the secondary of the pass transistor

A-004-004-003 (D)

When discussing a power supply the _____ resistance is equal to the output voltage divided by the total current drawn, including the current drawn by the bleeder resistor:

- A ideal
- B rectifier
- C differential
- D load

A-004-004-004 (D)

The regulation of long-term changes in the load resistance of a power supply is called:

- A active regulation
- B analog regulation
- C dynamic regulation
- D static regulation

A-004-004-005 (C)

The regulation of short-term changes in the load resistance of a power supply is called:

- A analog regulation
- B active regulation
- C dynamic regulation
- D static regulation

A-004-004-006 (B)

The dynamic regulation of a power supply is improved by increasing the value of:

- A the bleeder resistor
- B the output capacitor
- C the choke
- D the input capacitor

A-004-004-007 (B)

The output capacitor, in a power supply filter used to provide power for an SSB or CW transmitter, will give better dynamic regulation if:

- A it is placed in series with other capacitors
- B the output capacitance is increased
- C the negative terminal of the electrolytic capacitor is connected to the positive and the positive terminal to ground
- D a battery is placed in series with the output capacitor

A-004-004-008 (A)

In a regulated power supply, four diodes connected together in a BRIDGE act as:

- A a rectifier
- B equalization across the transformer
- C matching between the secondary of the power transformer and the filter
- D a tuning network

A-004-004-009 (D)

In a regulated power supply, components that conduct alternating current at the input before the transformer and direct current before the output are:

- A capacitors
- B diodes
- C chokes
- D fuses

A-004-004-010 (C)

In a regulated power supply, the output of the electrolytic filter capacitor is connected to the:

- A solid-state by-pass circuit
- B matching circuit for the load
- C voltage regulator
- D pi filter

A-004-004-011 (D)

In a regulated power supply, a diode connected across the input and output terminals of a regulator is used to:

- A provide an RF by-pass for the voltage control
- B provide additional capacity
- C protect the regulator from voltage fluctuations in the primary of the transformer
- D protect the regulator from reverse voltages

A-005-001-001 (B)

How is the positive feedback coupled to the input in a Hartley oscillator?

- A Through a neutralizing capacitor
- B Through a tapped coil
- C Through a capacitive divider
- D Through link coupling

A-005-001-002 (A)

How is positive feedback coupled to the input in a Colpitts oscillator?

- A Through a capacitive divider
- B Through a tapped coil
- C Through a neutralizing capacitor
- D Through a link coupling

A-005-001-003 (C)

How is positive feedback coupled to the input in a Pierce oscillator?

- A Through link coupling
- B Through a tapped coil
- C Through capacitive coupling
- D Through a neutralizing capacitor

A-005-001-004 (D)

Why is the Colpitts oscillator circuit commonly used in a VFO?

- A It can be used with or without crystal lock-in
- B The frequency is a linear function with load impedance
- C It has high output power
- D It is stable