

A-002-009-003 (D)

What occurs when an excessive amount of signal energy reaches the mixer circuit?

- A Automatic limiting occurs
- B A beat frequency is generated
- C Mixer blanking occurs
- D Spurious signals are generated

A-002-009-004 (D)

In a frequency multiplier circuit, the input signal is coupled to the base of a transistor through a capacitor. A radio frequency choke is connected between the base of the transistor and ground. The capacitor is:

- A part of the input tuned circuit
- B a by-pass for the circuit
- C part of the output tank circuit
- D a DC blocking capacitor

A-002-009-005 (A)

A frequency multiplier circuit must be operated in:

- A class C
- B class AB
- C class B
- D class A

A-002-009-006 (A)

In a frequency multiplier circuit, an inductance (L1) and a variable capacitor (C2) are connected in series between VCC+ and ground. The collector of a transistor is connected to a tap on L1. The purpose of the variable capacitor is to:

- A tune L1 to the desired harmonic
- B by-pass RF
- C tune L1 to the frequency applied to the base
- D provide positive feedback

A-002-009-007 (C)

In a frequency multiplier circuit, an inductance (L1) and a variable capacitor (C2) are connected in series between VCC+ and ground. The collector of a transistor is connected to a tap on L1. A fixed capacitor (C3) is connected between the VCC+ side of L1 and ground. The purpose of C3 is to:

- A resonate with L1
- B by-pass any audio components
- C provide an RF ground at the VCC connection point of L1
- D form a pi filter with L1 and C2

A-002-009-008 (D)

In a frequency multiplier circuit, an inductance (L1) and a variable capacitor (C2) are connected in series between VCC+ and ground. The collector of a transistor is connected to a tap on L1. C2 in conjunction with L1 operate as a:

- A frequency divider
- B voltage divider
- C voltage doubler
- D frequency multiplier

A-002-009-009 (D)

In a circuit where the components are tuned to resonate at a higher frequency than applied, the circuit is most likely a:

- A a VHF/UHF amplifier
- B a linear amplifier
- C a frequency divider
- D a frequency multiplier

A-002-009-010 (C)

In a frequency multiplier circuit, an inductance (L1) and a variable capacitor (C2) are connected in series between VCC+ and ground. The collector of a transistor is connected to a tap on L1. A fixed capacitor (C3) is connected between the VCC+ side of L1 and ground. C3 is a:

- A tuning capacitor
- B coupling capacitor
- C RF by-pass capacitor
- D DC blocking capacitor

A-002-009-011 (A)

What stage in a transmitter would change a 5.3-MHz input signal to 14.3 MHz?

- A A mixer
- B A linear translator
- C A frequency multiplier
- D A beat frequency oscillator

A-002-010-001 (D)

What is a NAND gate?

- A A circuit that produces a logic "1" at its output only when all inputs are logic "1"
- B A circuit that produces a logic "0" at its output if some but not all of its inputs are logic "1"
- C A circuit that produces a logic "0" at its output only when all inputs are logic "0"
- D A circuit that produces a logic "0" at its output only when all inputs are logic "1"

A-002-010-002 (B)

What is an OR gate?

- A A circuit that produces a logic "0" at its output if any input is logic "1"
- B A circuit that produces a logic "1" at its output if any input is logic "1"
- C A circuit that produces a logic "0" at its output if all inputs are logic "1"
- D A circuit that produces logic "1" at its output if all inputs are logic "0"

A-002-010-003 (D)

What is a NOR gate?

- A A circuit that produces a logic "0" at its output only if all inputs are logic "0"
- B A circuit that produces a logic "1" at its output only if all inputs are logic "1"
- C A circuit that produces a logic "1" at its output if some but not all of its inputs are logic "1"
- D A circuit that produces a logic "0" at its output if any or all inputs are logic "1"

A-002-010-004 (C)

What is a NOT gate (also known as an INVERTER)?

- A A circuit that allows data transmission only when its input is high
- B A circuit that produces a logic "1" at its output when the input is logic "1"
- C A circuit that produces a logic "0" at its output when the input is logic "1"
- D A circuit that does not allow data transmission when its input is high

A-002-010-005 (B)

What is an EXCLUSIVE OR gate?

- A A circuit that produces a logic "1" at its output when all of the inputs are logic "0"
- B A circuit that produces a logic "1" at its output when only one of the inputs is logic "1"
- C A circuit that produces a logic "0" at its output when only one of the inputs is logic "1"
- D A circuit that produces a logic "1" at its output when all of the inputs are logic "1"

A-002-010-006 (C)

What is an EXCLUSIVE NOR gate?

- A A circuit that produces a logic "1" at its output when only one of the inputs are logic "1"
- B A circuit that produces a logic "0" at its output when all of the inputs are logic "1"
- C A circuit that produces a logic "1" at its output when all of the inputs are logic "1"
- D A circuit that produces a logic "1" at its output when only one of the inputs is logic "0"

A-002-010-007 (B)

What is an AND gate?

- A A circuit that produces a logic "1" at its output if all inputs are logic "0"
- B A circuit that produces a logic "1" at its output only if all its inputs are logic "1"
- C A circuit that produces a logic "1" at the output if at least one input is a logic "0"
- D A circuit that produces a logic "1" at its output only if one of its inputs is logic "1"

A-002-010-008 (D)

What is a flip-flop circuit?

- A A binary sequential logic element with eight stable states
- B A binary sequential logic element with four stable states
- C A binary sequential logic element with one stable state
- D A binary sequential logic element with two stable states

A-002-010-009 (D)

What is a bistable multivibrator?

- A An OR gate
- B An AND gate
- C A clock
- D A flip-flop

A-002-010-010 (D)

What type of digital logic is also known as a latch?

- A A decade counter
- B An OR gate
- C An op-amp
- D A flip-flop

A-002-010-011 (D)

In a multivibrator circuit, when one transistor conducts, the other is:

- A saturated
- B reverse-biased
- C forward-biased
- D cut off

A-002-011-001 (D)

What is a crystal lattice filter?

- A A filter with wide bandwidth and shallow skirts made using quartz crystals
- B An audio filter made with four quartz crystals that resonate at 1 kHz intervals
- C A power supply filter made with interlaced quartz crystals
- D A filter with narrow bandwidth and steep skirts made using quartz crystals

A-002-011-002 (A)

What factor determines the bandwidth and response shape of a crystal lattice filter?

- A The relative frequencies of the individual crystals
- B The centre frequency chosen for the filter
- C The gain of the RF stage following the filter
- D The amplitude of the signals passing through the filter

A-002-011-003 (D)

For single-sideband phone emissions, what would be the bandwidth of a good crystal lattice filter?

- A 15 kHz
- B 500 Hz
- C 6 kHz
- D 2.4 kHz

A-002-011-004 (A)

The main advantage of a crystal oscillator over a tuned LC oscillator is:

- A much greater frequency stability
- B longer life under severe operating use
- C freedom from harmonic emissions
- D simplicity

A-002-011-005 (D)

A quartz crystal filter is superior to an LC filter for narrow bandpass applications because of the:

- A crystal's low Q
- B LC circuit's high Q
- C crystal's simplicity
- D crystal's high Q

A-002-011-006 (B)

Piezoelectricity is generated by:

- A moving a magnet near a crystal
- B deforming certain crystals
- C touching crystals with magnets
- D adding impurities to a crystal

A-002-011-007 (B)

Electrically, what does a crystal look like?

- A A variable tuned circuit
- B A very high Q tuned circuit
- C A very low Q tuned circuit
- D A variable capacitance

A-002-011-008 (A)

Crystals are sometimes used in a circuit which has an output close to an integral multiple of the crystal frequency. This circuit is called:

- A an overtone oscillator
- B a crystal multiplier
- C a crystal lattice
- D a crystal ladder

A-002-011-009 (D)

Which of the following properties does not apply to a crystal when used in an oscillator circuit?

- A Good frequency stability
- B Very low noise because of high Q
- C Good frequency accuracy
- D High power output

A-002-011-010 (C)

Crystal oscillators, filters and microphones depend upon which principle?

- A Ferro-resonance
- B Overtone effect
- C Piezoelectric effect
- D Hertzberg effect

A-002-011-011 (D)

Crystals are not applicable to which of the following?

- A Microphones
- B Lattice filters
- C Oscillators
- D Active filters

A-002-012-001 (D)

What are the three general groupings of filters?

- A Hartley, Colpitts and Pierce
- B Audio, radio and capacitive
- C Inductive, capacitive and resistive
- D High-pass, low-pass and band-pass

A-002-012-002 (A)

What are the distinguishing features of a Butterworth filter?

- A It has a maximally flat response over its pass-band
- B The product of its series and shunt-element impedances is a constant for all frequencies
- C It only requires conductors
- D It only requires capacitors

A-002-012-003 (B)

Which filter type is described as having ripple in the passband and a sharp cutoff?

- A A Butterworth filter
- B A Chebyshev filter
- C An active LC filter
- D A passive op-amp filter

A-002-012-004 (A)

What are the distinguishing features of a Chebyshev filter?

- A It allows ripple in the passband in return for steeper skirts
- B It requires only inductors
- C It requires only capacitors
- D It has a maximally flat response in the passband

A-002-012-005 (B)

Resonant cavities are used by amateurs as a:

- A high-pass filter above 30 MHz
- B narrow bandpass filter at VHF and higher frequencies
- C power line filter
- D low-pass filter below 30 MHz

A-002-012-006 (D)

On VHF and above, 1/4 wavelength coaxial cavities are used to give protection from high-level signals. For a frequency of approximately 50 MHz, the diameter of such a device would be about 10 cm (4 in). What would be its approximate length?

- A 0.6 metres (2 ft)
- B 2.4 metres (8 ft)
- C 3.7 metres (12 ft)
- D 1.5 metres (5 ft)

A-002-012-007 (A)

A device which helps with receiver overload and spurious responses at VHF, UHF and above may be installed in the receiver front end. It is called a:

- A helical resonator
- B diplexer
- C directional coupler
- D duplexer

A-002-012-008 (A)

Where you require bandwidth at VHF and higher frequencies about equal to a television channel, a good choice of filter is the:

- A none of the other answers
- B resonant cavity
- C Butterworth
- D Chebyshev

A-002-012-009 (D)

What is the primary advantage of the Butterworth filter over the Chebyshev filter?

- A It allows ripple in the passband in return for steeper skirts
- B It requires only inductors
- C It requires only capacitors
- D It has maximally flat response over its passband

A-002-012-010 (B)

What is the primary advantage of the Chebyshev filter over the Butterworth filter?

- A It has maximally flat response over the passband
- B It allows ripple in the passband in return for steeper skirts
- C It requires only capacitors
- D It requires only inductors

A-002-012-011 (D)

Which of the following filter types is not suitable for use at audio and low radio frequencies?

- A Elliptical
- B Chebyshev
- C Butterworth
- D Cavity

A-003-001-001 (C)

What is the easiest amplitude dimension to measure by viewing a pure sine wave on an oscilloscope?

- A RMS voltage
- B Average voltage
- C Peak-to-peak voltage
- D Peak voltage

A-003-001-002 (B)

What is the RMS value of a 340 volt peak-to-peak pure sine wave?

- A 300 volts
- B 120 volts
- C 170 volts
- D 240 volts

A-003-001-003 (D)

What is the equivalent to the RMS value of an AC voltage?

- A The AC voltage found by taking the square root of the peak AC voltage
- B The DC voltage causing the same heating of a given resistor as the peak AC voltage
- C The AC voltage found by taking the square root of the average AC value
- D The AC voltage causing the same heating of a given resistor as a DC voltage of the same value

A-003-001-004 (B)

If the peak value of a 100 Hz sinusoidal waveform is 20 volts, the RMS value is:

- A 16.38 volts
- B 14.14 volts
- C 28.28 volts
- D 7.07 volts

A-003-001-005 (B)

In applying Ohm's law to AC circuits, current and voltage values are:

- A none of the proposed answers
- B peak values times 0.707
- C average values
- D average values times 1.414

A-003-001-006 (C)

The effective value of a sine wave of voltage or current is:

- A 100% of the maximum value
- B 63.6% of the maximum value
- C 70.7% of the maximum value
- D 50% of the maximum value

A-003-001-007 (D)

AC voltmeter scales are usually calibrated to read:

- A peak voltage
- B instantaneous voltage
- C average voltage
- D RMS voltage

A-003-001-008 (B)

An AC voltmeter is calibrated to read the:

- A peak value
- B effective value
- C peak-to-peak value
- D average value

A-003-001-009 (C)

Which AC voltage value will produce the same amount of heat as a DC voltage, when applied to the same resistance?

- A The peak value
- B The peak-to-peak value
- C The RMS value
- D The average value

A-003-001-010 (B)

What is the peak-to-peak voltage of a sine wave that has an RMS voltage of 120 volts?

- A 204.8 volts
- B 339.5 volts
- C 84.8 volts
- D 169.7 volts

A-003-001-011 (A)

A sine wave of 17 volts peak is equivalent to how many volts RMS?

- A 12 volts
- B 24 volts
- C 34 volts
- D 8.5 volts

A-003-002-001 (C)

The power supplied to the antenna transmission line by a transmitter during an RF cycle at the highest crest of the modulation envelope is known as:

- A carrier power
- B full power
- C peak-envelope power
- D mean power

A-003-002-002 (C)

To compute one of the following, multiply the peak-envelope voltage by 0.707 to obtain the RMS value, square the result and divide by the load resistance. Which is the correct answer?

- A ERP
- B power factor
- C PEP
- D PIV

A-003-002-003 (C)

Peak-Envelope Power (PEP) for SSB transmission is:

- A equal to the RMS power
- B a hypothetical measurement
- C Peak-Envelope Voltage (PEV) multiplied by 0.707, squared and divided by the load resistance
- D peak-voltage multiplied by peak current

A-003-002-004 (C)

The formula to be used to calculate the power output of a transmitter into a resistor load using a voltmeter is:

- A $P = EI \cos 0$
- B $P = IR$
- C $P = (E \text{ exponent } 2) / R$
- D $P = EI/R$