

A-005-009-009 (D)

What is direct-sequence spread spectrum?

- A The carrier is amplitude modulated over a range called the spread
- B The carrier is frequency-companded
- C The carrier is altered in accordance with a pseudo-random list of channels
- D The carrier is phase-shifted by a fast binary bit stream

A-005-009-010 (C)

Why are received spread-spectrum signals so resistant to interference?

- A If interference is detected by the receiver, it will signal the transmitter to change frequencies
- B The high power used by a spread-spectrum transmitter keeps its signal from being easily overpowered
- C Signals not using the spectrum-spreading algorithm are suppressed in the receiver
- D The receiver is always equipped with a special digital signal processor (DSP) interference filter

A-005-009-011 (D)

How does the spread-spectrum technique of frequency hopping work?

- A If interference is detected by the receiver, it will signal the transmitter to change frequency
- B If interference is detected by the receiver, it will signal the transmitter to wait until the frequency is clear
- C A pseudo-random bit stream is used to shift the phase of an RF carrier very rapidly in a particular sequence
- D The frequency of an RF carrier is changed very rapidly according to a particular pseudo-random sequence

A-006-001-001 (C)

What are the advantages of the frequency conversion process in a superheterodyne receiver?

- A Automatic soft-limiting and automatic squelching
- B Automatic squelching and increased sensitivity
- C Increased selectivity and optimal tuned circuit design
- D Automatic detection in the RF amplifier and increased sensitivity

A-006-001-002 (A)

What factors should be considered when selecting an intermediate frequency?

- A Image rejection and responses to unwanted signals
- B Noise figure and distortion
- C Interference to other services
- D Cross-modulation distortion and interference

A-006-001-003 (B)

One of the greatest advantages of the double-conversion over the single-conversion receiver is that it:

- A produces a louder signal at the output
- B greater reduction of image interference for a given front end selectivity
- C is much more stable
- D is much more sensitive

A-006-001-004 (A)

In a communications receiver, a crystal filter would be located in the:

- A IF circuits
- B local oscillator
- C audio output stage
- D detector

A-006-001-005 (B)

A multiple conversion superheterodyne receiver is more susceptible to spurious responses than a single-conversion receiver because of the:

- A AGC being forced to work harder causing the stages concerned to overload
- B additional oscillators and mixing frequencies involved in the design
- C poorer selectivity in the IF caused by the multitude of frequency changes
- D greater sensitivity introducing higher levels of RF to the receiver

A-006-001-006 (C)

In a dual-conversion superheterodyne receiver what are the respective aims of the first and second conversion:

- A selectivity and dynamic range
- B image rejection and noise figure
- C image rejection and selectivity
- D selectivity and image rejection

A-006-001-007 (D)

Which stage of a receiver has its input and output circuits tuned to the received frequency?

- A The local oscillator
- B The audio frequency amplifier
- C The detector
- D The RF amplifier

A-006-001-008 (D)

Which stage of a superheterodyne receiver lies between a tuneable stage and a fixed tuned stage?

- A Radio frequency amplifier
- B Intermediate frequency amplifier
- C Local oscillator
- D Mixer

A-006-001-009 (B)

A single conversion receiver with a 9 MHz IF has a local oscillator operating at 16 MHz. The frequency it is tuned to is:

- A 9 MHz
- B 7 MHz
- C 16 MHz
- D 21 MHz

A-006-001-010 (A)

A double conversion receiver designed for SSB reception has a beat frequency oscillator and:

- A two IF stages and two local oscillators
- B one IF stage and one local oscillator
- C two IF stages and three local oscillators
- D two IF stages and one local oscillator

A-006-001-011 (C)

The advantage of a double conversion receiver over a single conversion receiver is that it:

- A is a more sensitive receiver
- B produces a louder audio signal
- C suffers less from image interference for a given front end sensitivity
- D does not drift off frequency

A-006-002-001 (D)

The mixer stage of a superheterodyne receiver is used to:

- A allow a number of IF frequencies to be used
- B remove image signals from the receiver
- C produce an audio frequency for the speaker
- D change the frequency of the incoming signal to that of the IF

A-006-002-002 (C)

A superheterodyne receiver designed for SSB reception must have a beat-frequency oscillator (BFO) because:

- A it reduces the pass-band of the IF stages
- B it beats with the receiver carrier to produce the missing sideband
- C the suppressed carrier must be replaced for detection
- D it phases out the unwanted sideband signal

A-006-002-003 (C)

The first mixer in the receiver mixes the incoming signal with the local oscillator to produce:

- A a radio frequency
- B a high frequency oscillator (HFO) frequency
- C an intermediate frequency
- D an audio frequency

A-006-002-004 (B)

If the incoming signal to the mixer is 3 600 kHz and the first IF is 9 MHz, at which one of the following frequencies would the local oscillator (LO) operate?

- A 21 600 kHz
- B 5 400 kHz
- C 3 400 kHz
- D 10 600 kHz

A-006-002-005 (C)

The BFO is off-set slightly (500 - 1 500 Hz) from the incoming signal to the detector. This is required:

- A to provide additional amplification
- B to protect the incoming signal from interference
- C to beat with the incoming signal
- D to pass the signal without interruption

A-006-002-006 (C)

It is very important that the oscillators contained in a superheterodyne receiver are:

- A stable and sensitive
- B selective and spectrally pure
- C stable and spectrally pure
- D sensitive and selective

A-006-002-007 (A)

In a superheterodyne receiver, a stage before the IF amplifier has a variable capacitor in parallel with a trimmer capacitor and an inductance. The variable capacitor is for:

- A tuning of the local oscillator (LO)
- B tuning both the antenna and the BFO
- C tuning of the beat-frequency oscillator (BFO)
- D tuning both the antenna and the LO

A-006-002-008 (A)

In a superheterodyne receiver without an RF amplifier, the input to the mixer stage has a variable capacitor in parallel with an inductance. The variable capacitor is for:

- A tuning the receiver preselector to the reception frequency
- B tuning both the antenna and the beat-frequency oscillator
- C tuning the beat-frequency oscillator
- D tuning both the antenna and the local oscillator

A-006-002-009 (B)

What receiver stage combines a 14.25-MHz input signal with a 13.795-MHz oscillator signal to produce a 455-kHz intermediate frequency (IF) signal?

- A Multiplier
- B Mixer
- C BFO
- D VFO

A-006-002-010 (D)

Which two stages in a superheterodyne receiver have input tuned circuits tuned to the same frequency?

- A IF and local oscillator
- B RF and IF
- C RF and local oscillator
- D RF and first mixer

A-006-002-011 (B)

The mixer stage of a superheterodyne receiver:

- A demodulates SSB signals
- B produces an intermediate frequency
- C produces spurious signals
- D acts as a buffer stage

A-006-003-001 (B)

What is meant by the noise floor of a receiver?

- A The amount of noise generated by the receiver local oscillator
- B The weakest signal that can be detected above the receiver internal noise
- C The weakest signal that can be detected under noisy atmospheric conditions
- D The minimum level of noise that will overload the receiver RF amplifier stage

A-006-003-002 (C)

Which of the following is a purpose of the first IF amplifier stage in a receiver?

- A To increase dynamic response
- B To improve noise figure performance
- C To improve selectivity and gain
- D To tune out cross-modulation distortion

A-006-003-003 (D)

How much gain should be used in the RF amplifier stage of a receiver?

- A As much gain as possible, short of self-oscillation
- B It depends on the amplification factor of the first IF stage
- C Sufficient gain to keep weak signals below the noise of the first mixer stage
- D Sufficient gain to allow weak signals to overcome noise generated in the first mixer stage

A-006-003-004 (D)

What is the primary purpose of an RF amplifier in a receiver?

- A To vary the receiver image rejection by using the AGC
- B To develop the AGC voltage
- C To provide most of the receiver gain
- D To improve the receiver noise figure

A-006-003-005 (C)

How is receiver sensitivity often expressed for UHF FM receivers?

- A Noise Figure in decibels
- B Overall gain in decibels
- C RF level for 12 dB SINAD
- D RF level for a given Bit Error Rate (BER)

A-006-003-006 (A)

What is the term used for the decibel difference (or ratio) between the largest tolerable receiver input signal (without causing audible distortion products) and the minimum discernible signal (sensitivity)?

- A Dynamic range
- B Design parameter
- C Stability
- D Noise figure

A-006-003-007 (D)

The lower the receiver noise figure becomes, the greater will be the receiver's _____:

- A rejection of unwanted signals
- B selectivity
- C stability
- D sensitivity

A-006-003-008 (B)

The noise generated in a receiver of good design originates in the:

- A IF amplifier and detector
- B RF amplifier and mixer
- C detector and AF amplifier
- D BFO and detector

A-006-003-009 (B)

Why are very low noise figures relatively unimportant for a high frequency receiver?

- A Regardless of the front end, the succeeding stages when used on HF are very noisy
- B External HF noise, man-made and natural, are higher than the internal noise generated by the receiver
- C Ionospheric distortion of the received signal creates high noise levels
- D The use of SSB and CW on the HF bands overcomes the noise

A-006-003-010 (B)

The term which relates specifically to the amplitude levels of multiple signals that can be accommodated during reception is called:

- A noise figure
- B dynamic range
- C AGC
- D cross-modulation index

A-006-003-011 (C)

Normally, front-end selectivity is provided by the resonant networks both before and after the RF stage in a superheterodyne receiver. This whole section of the receiver is often referred to as the:

- A preamplifier
- B pass-selector
- C preselector
- D preamble

A-006-004-001 (D)

What audio shaping network is added at an FM receiver to restore proportionally attenuated lower audio frequencies?

- A A pre-emphasis network
- B An audio prescaler
- C A heterodyne suppressor
- D A de-emphasis network

A-006-004-002 (B)

What does a product detector do?

- A It detects cross-modulation products
- B It mixes an incoming signal with a locally generated carrier
- C It provides local oscillations for input to a mixer
- D It amplifies and narrows band-pass frequencies

A-006-004-003 (D)

Distortion in a receiver that only affects strong signals usually indicates a defect in or mis-adjustment of the:

- A IF amplifier
- B AF amplifier
- C RF amplifier
- D automatic gain control (AGC)

A-006-004-004 (B)

In a superheterodyne receiver with automatic gain control (AGC), as the strength of the signal increases, the AGC:

- A introduces limiting
- B reduces the receiver gain
- C increases the receiver gain
- D distorts the signal

A-006-004-005 (B)

The amplified IF signal is applied to the _____ stage in a superheterodyne receiver:

- A LO
- B detector
- C RF amplifier
- D audio output

A-006-004-006 (A)

The low-level output of a detector is:

- A applied to the AF amplifier
- B grounded via the chassis
- C fed directly to the speaker
- D applied to the RF amplifier

A-006-004-007 (B)

The overall output of an AM/CW/SSB receiver can be adjusted by means of manual controls on the receiver or by use of a circuit known as:

- A automatic load control
- B automatic gain control
- C automatic frequency control
- D inverse gain control

A-006-004-008 (D)

AGC voltage is applied to the:

- A AF and IF amplifiers
- B RF and AF amplifiers
- C detector and AF amplifiers
- D RF and IF amplifiers

A-006-004-009 (D)

AGC is derived in a receiver from one of two circuits. Depending on the method used, it is called:

- A RF derived or audio derived
- B IF derived or RF derived
- C detector derived or audio derived
- D IF derived or audio derived

A-006-004-010 (D)

Which two variables primarily determine the behaviour of an automatic gain control (AGC) loop?

- A Blanking level and slope
- B Slope and bandwidth
- C Clipping level and hang time
- D Threshold and decay time

A-006-004-011 (A)

What circuit combines signals from an IF amplifier stage and a beat-frequency oscillator (BFO), to produce an audio signal?

- A A product detector circuit
- B An AGC circuit
- C A power supply circuit
- D A VFO circuit

A-006-005-001 (C)

What part of a superheterodyne receiver determines the image rejection ratio of the receiver?

- A AGC loop
- B IF filter
- C RF amplifier pre-selector
- D Product detector

A-006-005-002 (A)

What is the term for the reduction in receiver sensitivity caused by a strong signal near the received frequency?

- A Desensitization
- B Cross-modulation interference
- C Squelch gain rollback
- D Quieting

A-006-005-003 (A)

What causes receiver desensitization?

- A Strong near frequency signals
- B Squelch gain adjusted too high
- C Squelch gain adjusted too low
- D Audio gain adjusted too low

A-006-005-004 (D)

What is one way receiver desensitization can be reduced?

- A Decrease the receiver squelch gain
- B Increase the receiver bandwidth
- C Increase the transmitter audio gain
- D Use a cavity filter

A-006-005-005 (D)

What causes intermodulation in an electronic circuit?

- A Too little gain
- B Positive feedback
- C Lack of neutralization
- D Nonlinear circuits or devices

A-006-005-006 (B)

Which of the following is an important reason for using a VHF intermediate frequency in an HF receiver?

- A To prevent the generation of spurious mixer products
- B To move the image response far away from the filter passband
- C To provide a greater tuning range
- D To tune out cross-modulation distortion

A-006-005-007 (C)

Intermodulation interference is produced by:

- A the high-voltage stages in the final amplifier of an amplitude or frequency-modulated transmitter
- B the mixing of more than one signal in the first or second intermediate frequency amplifiers of a receiver
- C the mixing of two or more signals in the front-end of a superheterodyne receiver
- D the interaction of products from high-powered transmitters in the area

A-006-005-008 (A)

Which of the following is NOT a direct cause of instability in a receiver?

- A Dial display accuracy
- B Mechanical rigidity
- C Feedback components
- D Temperature variations

A-006-005-009 (B)

Poor frequency stability in a receiver usually originates in the:

- A mixer
- B local oscillator and power supply
- C detector
- D RF amplifier

A-006-005-010 (B)

Poor dynamic range of a receiver can cause many problems when a strong signal appears within or near the front-end bandpass. Which of the following is NOT caused as a direct result?

- A Cross-modulation
- B Feedback
- C Desensitization
- D Intermodulation